

Assignment Report

Name : Shubham Santoshbhai Machhi

Batch : A04


Branch : Electronics (EL)

I.D. No. : 21EL006

College : Birla Vishwakarma Mahavidyalaya

1. Clock Divider :-


Verilog Code:

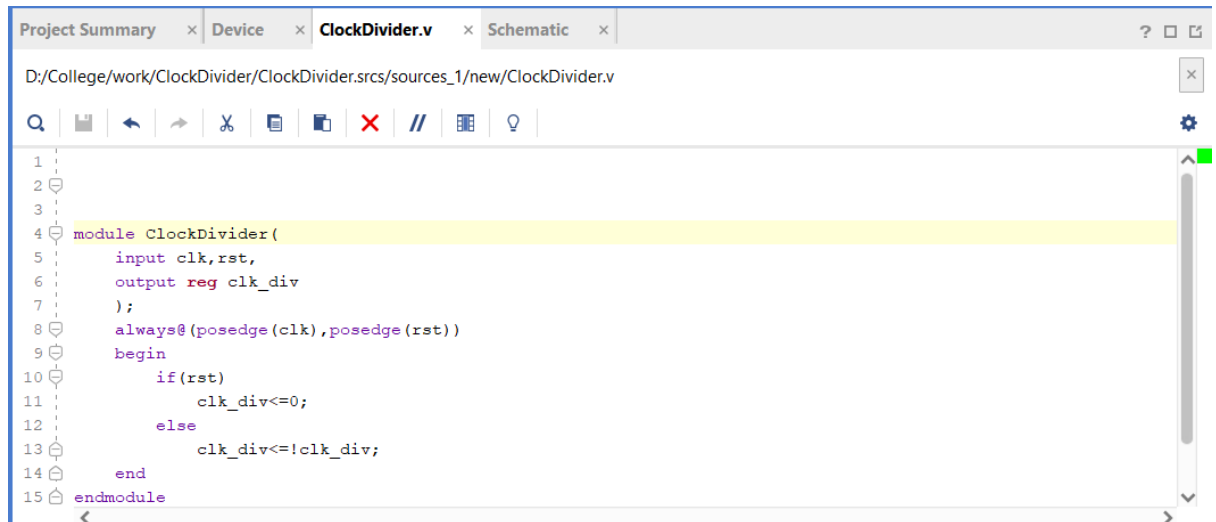

The screenshot shows a text editor window with the title bar 'Project Summary x Device x ClockDivider.v x Schematic x'. The file path is 'D:/College/work/ClockDivider/ClockDivider.srscs/sources_1/new/ClockDivider.v'. The code is as follows:

```
1 |
2 |
3 |
4 | module ClockDivider(
5 |     input clk,rst,
6 |     output reg clk_div
7 | );
8 | always@(posedge (clk),posedge (rst))
9 | begin
10 |     if(rst)
11 |         clk_div<=0;
12 |     else
13 |         clk_div<=!clk_div;
14 |     end
15 | endmodule
```


Test Bench:

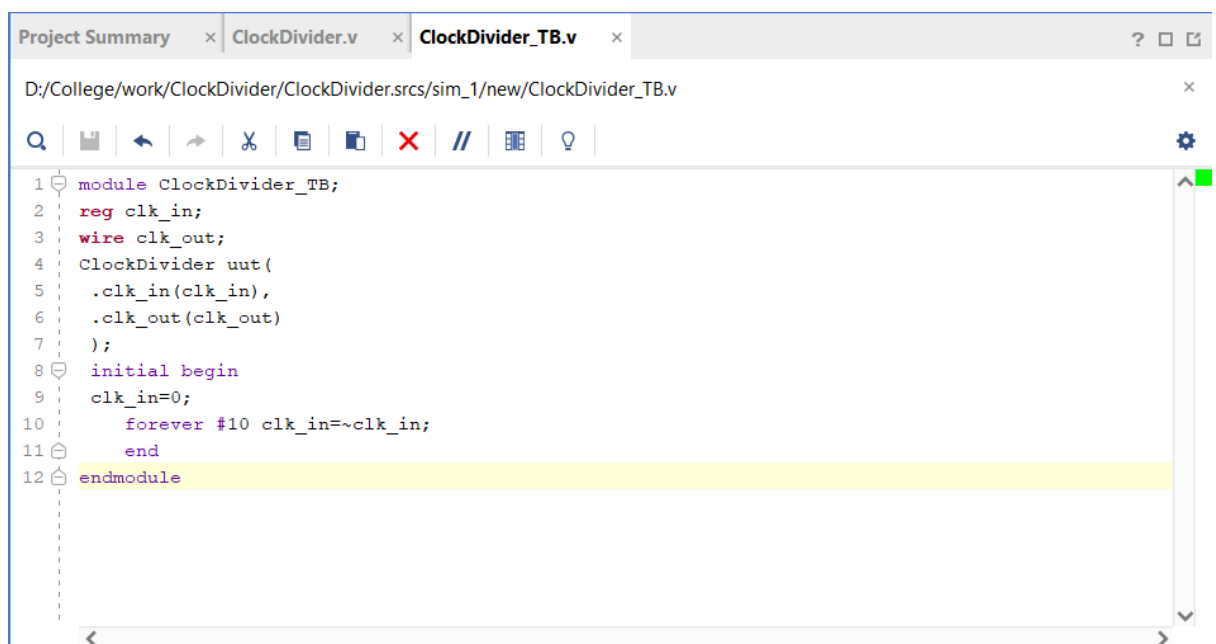

The screenshot shows a text editor window with the title bar 'Project Summary x ClockDivider.v x ClockDivider_TB.v x'. The file path is 'D:/College/work/ClockDivider/ClockDivider.srscs/sim_1/new/ClockDivider_TB.v'. The code is as follows:

```
1 | module ClockDivider_TB;
2 |     reg clk_in;
3 |     wire clk_out;
4 |     ClockDivider uut(
5 |         .clk_in(clk_in),
6 |         .clk_out(clk_out)
7 |     );
8 |     initial begin
9 |         clk_in=0;
10 |         forever #10 clk_in=~clk_in;
11 |     end
12 | endmodule
```

RTL Schematic:

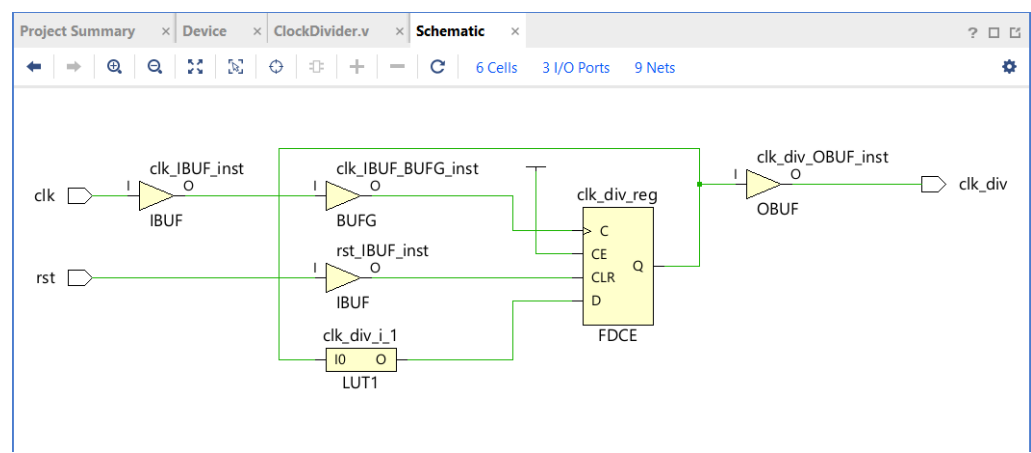

Synthesis Report:

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+-----+
| |BlackBox name |Instances |
+-----+-----+
+-----+-----+

Report Cell Usage:
+-----+-----+
|      |Cell |Count |
+-----+-----+
|1      |BUFG |    1|
|2      |LUT1 |    1|
|3      |FDCE |    1|
|4      |IBUF |    2|
|5      |OBUF |    1|
+-----+-----+

Report Instance Areas:
+-----+-----+-----+-----+
|      |Instance |Module |Cells |
+-----+-----+-----+-----+
|1      |top      |      |    6|
+-----+-----+-----+-----+
-----


Finished Writing Synthesis Report : Time (s): cpu = 00:00:13 ; elapsed = 00:00:13 .
-----
```

Power Report:

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: 2.114 W
Design Power Budget: Not Specified
Process: typical
Power Budget Margin: N/A
Junction Temperature: 29.0°C
Thermal Margin: 56.0°C (29.5 W)
Ambient Temperature: 25.0 °C
Effective θ_{JA} : 1.9°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low
[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

2. Johnson Counter :-


Verilog Code:

```
1 module johnsonCounter#(parameter WIDTH=4)
2 (
3   input clk,
4   input rstn,
5   output reg [WIDTH-1:0]out,
6   integer i
7 );
8 always@(posedge clk)
9 begin
10   if(!rstn)
11     out<=1;
12   else
13     begin
14       out[WIDTH-1]<=~out[0];
15       for(i=0;i<WIDTH-1;i=i+1)
16       begin
17         out[i]<=out[i+1];
18       end
19     end
20 end
21 endmodule
```

Test Bench:

```
1 module JohnsonCounter_TB;
2   parameter WIDTH=4;
3   reg clk;
4   reg rstn;
5   wire [WIDTH-1:0]out;
6   JohnsonCounter u0(.clk(clk),
7   .rstn(rstn),
8   .out(out));
9   always#10 clk=~clk;
10  initial
11  begin
12      {clk,rstn}<=0;
13      $monitor("T=%0t out=%b", $time, out);
14      repeat(2)@(posedge clk);
15      rstn<=1;
16      repeat(15)@(posedge clk);
17      $finish;
18  end
19  endmodule
20
```

RTL Schematic:

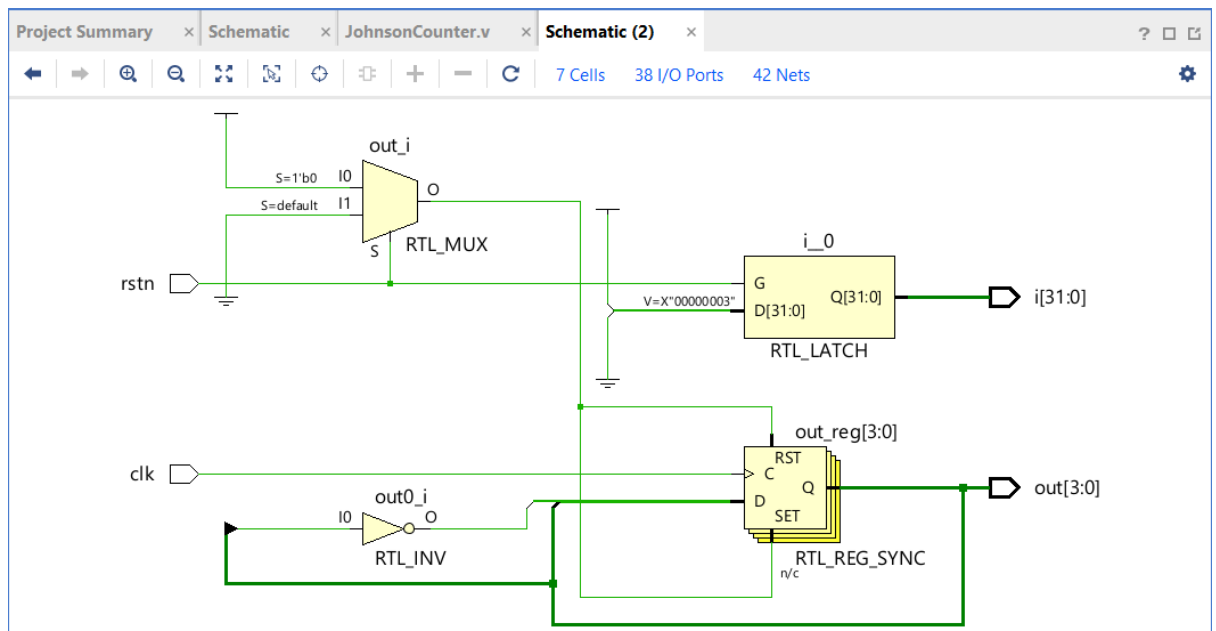

Synthesis Report:

```
-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
++-----+
| |BlackBox name |Instances |
++-----+
++-----+

Report Cell Usage:
+-----+-----+-----+
|      |Cell |Count |
+-----+-----+-----+
|1      |BUFG |      1|
|2      |LUT1 |      2|
|3      |FDRE |      3|
|4      |FDSE |      1|
|5      |IBUF |      2|
|6      |OBUF |     36|
+-----+-----+-----+

Report Instance Areas:
+-----+-----+-----+-----+
|      |Instance |Module |Cells |
+-----+-----+-----+-----+
|1      |top      |      |    45|
+-----+-----+-----+-----+
-----

Finished Writing Synthesis Report : Time (s): cpu = 00:00:16 ; elapsed = 00:00:16 .
```

Power Report:

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:	1.099 W
Design Power Budget:	Not Specified
Process:	typical
Power Budget Margin:	N/A
Junction Temperature:	27.1°C
Thermal Margin:	57.9°C (30.6 W)
Ambient Temperature:	25.0 °C
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

Dynamic:	1.016 W	(92%)
Signals:	0.050 W	(5%)
Logic:	0.009 W	(1%)
I/O:	0.957 W	(94%)
Device Static:	0.083 W	(8%)

3. Ring Counter :-


Verilog Code:

```
module ringcounter(clk, rst, count);
    input clk, rst;
    output [5:0] count;
    wire clk, rst;
    reg [5:0] count = 6'b1;
    always @ ( posedge clk )
        begin
            if ( ~rst )
                begin
                    count <= count << 1;
                    count[0] <= count[5];
                end
            end
        end
    always @ ( posedge rst )
        begin
            count <= 6'b1;
        end
end
```

Test Bench:

```
module RingCounter_TB;
    reg Clock;
    reg Reset;
    wire [3:0] Count_out;
    ring_counter uut (
        .Clock(Clock),
        .Reset(Reset),
        .Count_out(Count_out)
    );
    initial Clock = 0;
    always #10 Clock = ~Clock;
    initial
    begin
        Reset = 1;
        #50;
        Reset = 0;
    end
endmodule
```

RTL Schematic:

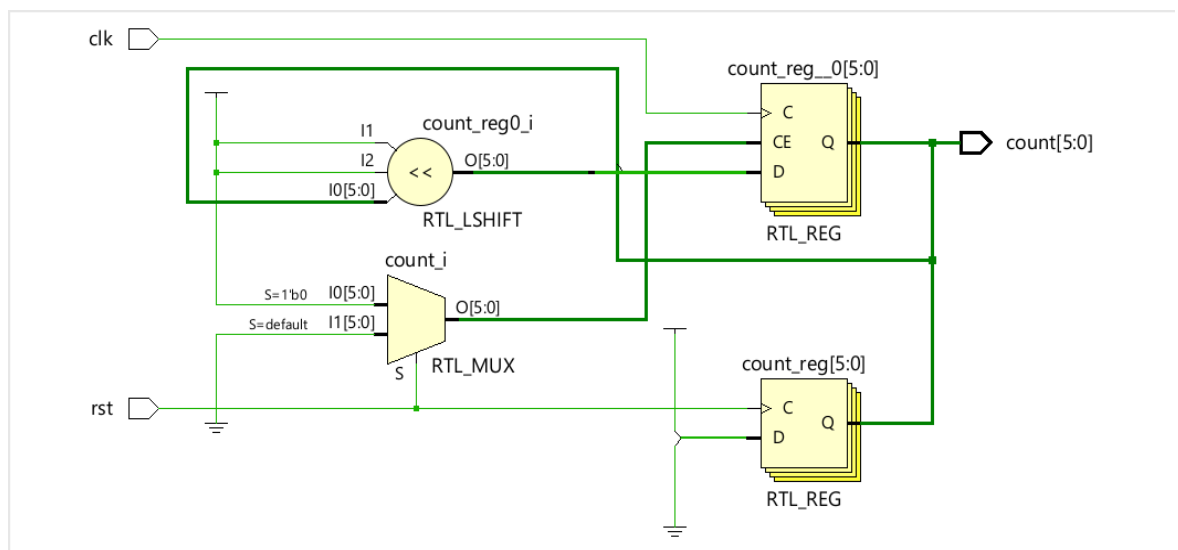

Synthesis Report:

Start Writing Synthesis Report

Report BlackBoxes:

```
+-----+
| |BlackBox name |Instances |
+-----+
+-----+
```

Report Cell Usage:

```
+-----+
|      |Cell |Count |
+-----+
| 1    |BUFG |    2|
| 2    |LUT1 |    2|
| 3    |FDRE |   12|
| 4    |IBUF |    2|
| 5    |OBUF |    6|
+-----+
```

Report Instance Areas:

```
+-----+
|      |Instance |Module |Cells |
+-----+
| 1    |top      |      |   24|
+-----+
```

Finished Writing Synthesis Report : Time (s): cpu = 00:00:18 ; elapsed = 00:00:36


Power Report:

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: 0.1 W
Design Power Budget: Not Specified
Process: typical
Power Budget Margin: N/A
Junction Temperature: 25.2°C
Thermal Margin: 59.8°C (31.6 W)
Ambient Temperature: 25.0 °C
Effective θ_{JA} : 1.9°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

4. 5 Input Majority Circuit :-


Verilog Code:

```
module MajorityCircuit(  
    input [4:0] sw,  
    output led  
);  
    assign led=(sw[0] & sw[1] & sw[2]) |  
               (sw[0] & sw[1] & sw[3]) |  
               (sw[0] & sw[1] & sw[4]) |  
               (sw[0] & sw[2] & sw[3]) |  
               (sw[0] & sw[2] & sw[4]) |  
               (sw[0] & sw[3] & sw[4]) |  
               (sw[1] & sw[2] & sw[3]) |  
               (sw[1] & sw[2] & sw[4]) |  
               (sw[1] & sw[3] & sw[4]) |  
               (sw[2] & sw[3] & sw[4]);  
endmodule
```

Test Bench:

```
module MajorityCircuit_TB;
  reg [4:0] sw;
  wire led;
  majority_of_five cut (.sw(sw),.led(led));
  integer k;
  initial
  begin
    sw = 0;
    for (k=0; k<32; k=k+1)
      #20 sw = k;
      #20 $finish;
  end
endmodule
```

RTL Schematic:

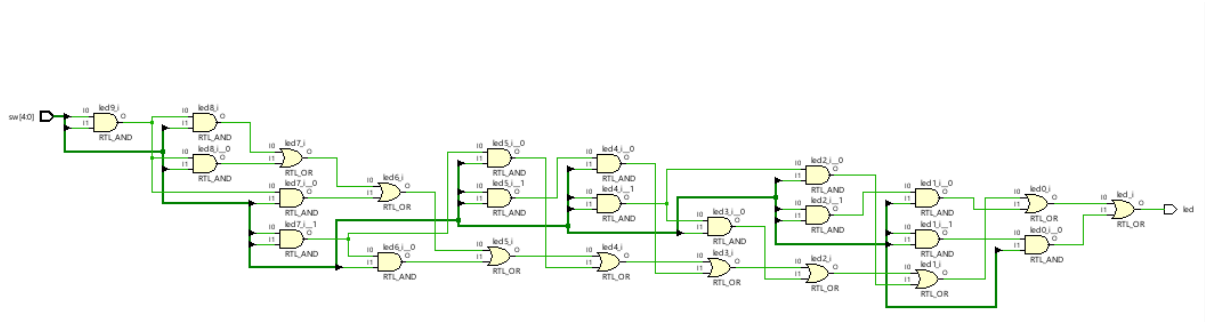

Synthesis Report:

```
-----
Start Writing Synthesis Report
-----


Report BlackBoxes:
+-----+
| BlackBox name | Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell | Count |
+-----+
| 1 | LUT5 | 1 |
| 2 | IBUF | 5 |
| 3 | OBUF | 1 |
+-----+

Report Instance Areas:
+-----+
| Instance | Module | Cells |
+-----+
| 1 | top | 1 | 7 |
+-----+

Finished Writing Synthesis Report : Time (s): cpu = 00:00:18 ; elapsed = 00:00:25
```

Power Report:

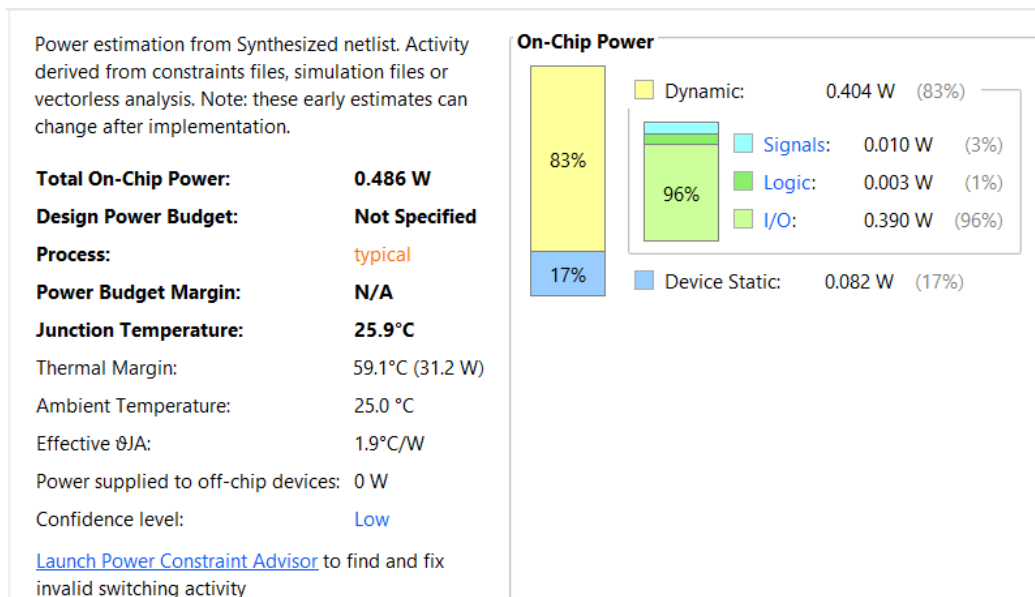

5. Parity Generator :-

Verilog Code:

Project Summary × Schematic × ParityGenerator.v ×

D:/College/work/ParityGenerator/ParityGenerator.srscs/sources_1/new/Par


🔍 📁 ↶ ↷ ✂ 📄 📄 ✖ // 📊 💡

```
1 module ParityGenerator(  
2     input x,y,z,  
3     output result);  
4     xor (result,x,y,z);  
5 endmodule
```

Test Bench:

```
1 module ParityGenerator_TB;
2     reg x,y,z;
3     wire result;
4     initial
5     begin
6         x = 0;
7         y = 0;
8         z = 0;
9         #100;
10        x = 0;
11        y = 0;
12        z = 1;
13        #100;
14        x = 0;
15        y = 1;
16        z = 0;
17        #100;
18        x = 0;
19        y = 1;
20        z = 1;
21        #100;
22        x = 1;
23        y = 0;
24        z = 0;
25        #100;
26        x = 1;
27        y = 0;
28        z = 1;
29        #100;
30        x = 1;
31        y = 1;
32        z = 0;
33        #100;
34        x = 1;
35        y = 1;
36        z = 1;
37        #100;
38    end
39 endmodule
40
```

RTL Schematic:

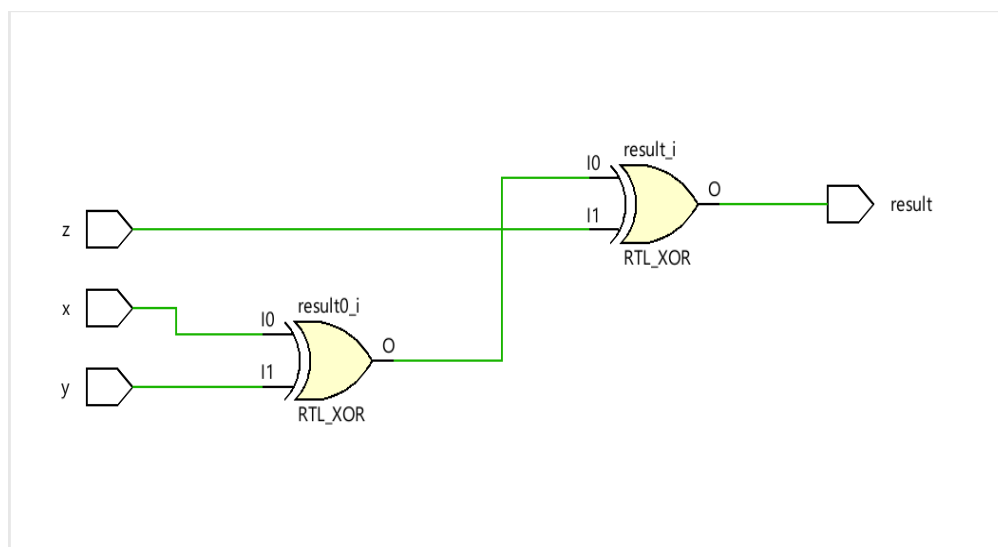

Synthesis Report:

```
-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-+-----+-----+
| |BlackBox name |Instances |
+-+-----+-----+
+-+-----+-----+

Report Cell Usage:
+-----+-----+
|      |Cell |Count |
+-----+-----+
|1      |LUT3 |    1|
|2      |IBUF |    3|
|3      |OBUF |    1|
+-----+-----+

Report Instance Areas:
+-----+-----+-----+-----+
|      |Instance |Module |Cells |
+-----+-----+-----+-----+
|1      |top      |      |    5|
+-----+-----+-----+-----+
-----

Finished Writing Synthesis Report : Time (s): cpu = 00:00:17 ; elapsed = 00:00:27
```

Power Report:

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:	0.672 W
Design Power Budget:	Not Specified
Process:	typical
Power Budget Margin:	N/A
Junction Temperature:	26.3°C
Thermal Margin:	58.7°C (31.0 W)
Ambient Temperature:	25.0 °C
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

Dynamic:	0.589 W	(88%)
Device Static:	0.082 W	(12%)
Signals:	0.016 W	(3%)
Logic:	0.003 W	(1%)
I/O:	0.570 W	(96%)

6. Binary To One Hot Encoder :-


Verilog Code:

```
module HotEncoder(  
    input x,y,z,  
    output [7:0]out  
);  
    assign out[0]=(~x&~y&~z);  
    assign out[1]=(~x&~y&z);  
    assign out[2]=(~x&y&~z);  
    assign out[3]=(~x&y&z);  
    assign out[4]=(x&~y&~z);  
    assign out[5]=(x&~y&z);  
    assign out[6]=(x&y&~z);  
    assign out[7]=(x&y&z);  
endmodule
```

Test Bench:

```
module HotEncoder_TB;  
    reg x,y,z;  
    wire[7:0]out;  
    HotEncoder DUT(x,y,z,out);  
    initial  
    begin  
        $monitor($time,"x=%b,y=%b,z=%b,out=%b",x,y,z,out);  
        x=0;y=0;z=0;  
        #100  
        x=0;y=0;z=1;  
        #100  
        x=0;y=1;z=0;  
        #100  
        x=1;y=1;z=1;  
        #100  
        $finish;  
    end  
endmodule
```

RTL Schematic:

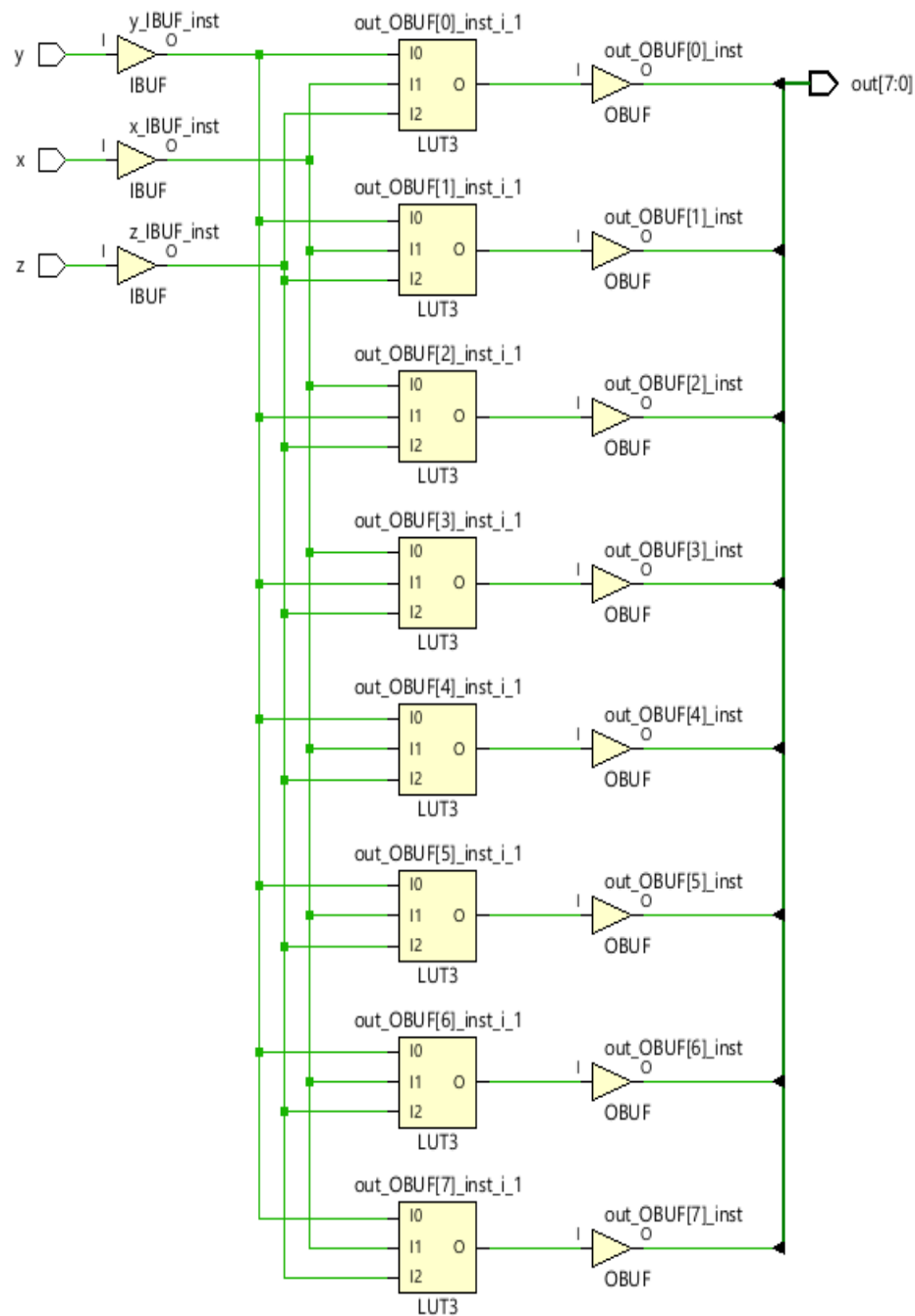

Synthesis Report:

```
-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-+-----+-----+
| |BlackBox name |Instances |
+-+-----+-----+
+-+-----+-----+

Report Cell Usage:
+-----+-----+
|      |Cell |Count |
+-----+-----+
|1      |LUT3 |      8|
|2      |IBUF |      3|
|3      |OBUF |      8|
+-----+-----+

Report Instance Areas:
+-----+-----+-----+-----+
|      |Instance |Module |Cells |
+-----+-----+-----+-----+
|1      |top      |      |    19|
+-----+-----+-----+-----+

-----
Finished Writing Synthesis Report : Time (s): cpu = 00:00:16 ; elapsed = 00:00:26
-----
```

Power Report:

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:	1.412 W
Design Power Budget:	Not Specified
Process:	typical
Power Budget Margin:	N/A
Junction Temperature:	27.7°C
Thermal Margin:	57.3°C (30.2 W)
Ambient Temperature:	25.0 °C
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

Dynamic:	1.328 W	(94%)
Device Static:	0.084 W	(6%)

Signals:	0.036 W	(3%)
Logic:	0.017 W	(1%)
I/O:	1.275 W	(96%)

7. 4 Bit BCD Synchronous Counter :-

Verilog Code:


```
module BCDCounter (
    input wire clk,
    input wire rst,
    output wire [3:0] bcd
);
    reg [3:0] count;
    always @(posedge clk or posedge rst) begin
        if (rst) begin
            count <= 4'b0000;
        end else begin
            if (count == 4'b1001) begin
                count <= 4'b0000;
            end else begin
                count <= count + 1;
            end
        end
    end
    assign bcd = count;
endmodule
```

Test Bench:

```
module BCDCounter_TB;

    reg clk;
    reg rst;
    wire [3:0] bcd;
    BCDCounter UUT (.clk(clk), .rst(rst), .bcd(bcd));
    initial begin
        clk = 0;
        rst = 0;
        #5 rst = 1;
        #5 rst = 0;
        repeat (20) begin
            #5 clk = ~clk;
        end
        $finish;
    end
    always begin
        #2 clk = ~clk;
    end
endmodule
```

RTL Schematic:

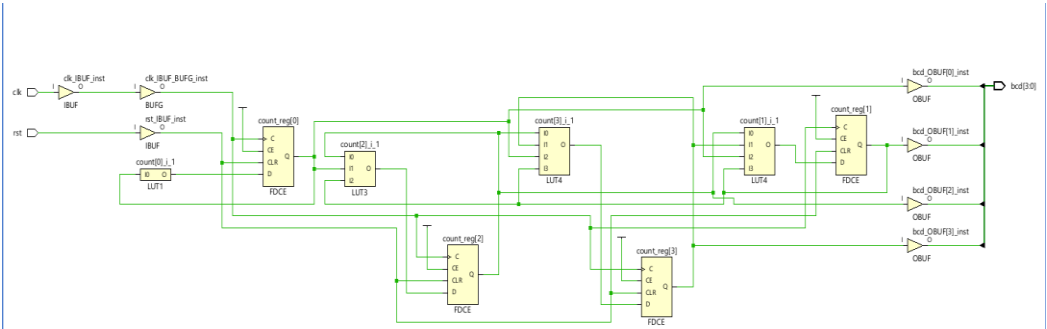

Synthesis Report:

```
-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+-----+
| |BlackBox name |Instances |
+-----+-----+
+-----+-----+

Report Cell Usage:
+-----+-----+-----+
|      |Cell |Count |
+-----+-----+-----+
|1      |BUFG |    1|
|2      |LUT1 |    1|
|3      |LUT3 |    1|
|4      |LUT4 |    2|
|5      |FDCE |    4|
|6      |IBUF |    2|
|7      |OBUF |    4|
+-----+-----+-----+

Report Instance Areas:
+-----+-----+-----+-----+
|      |Instance |Module |Cells |
+-----+-----+-----+-----+
|1      |top      |      |    15|
+-----+-----+-----+-----+

-----
Finished Writing Synthesis Report : Time (s): cpu = 00:00:14 ; elapsed = 00:00:26
-----
```


Power Report:

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:	3.661 W
Design Power Budget:	Not Specified
Process:	typical
Power Budget Margin:	N/A
Junction Temperature:	31.9°C
Thermal Margin:	53.1°C (28.0 W)
Ambient Temperature:	25.0 °C
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

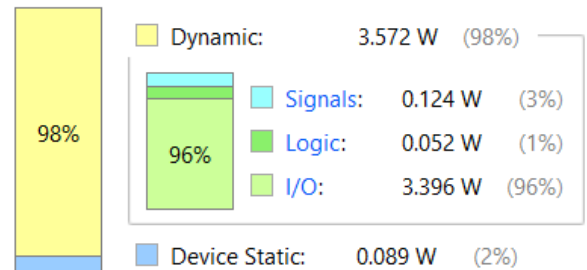

8. 4-Bit Carry Look Ahead Adder :-

Verilog Code:

```
module LookAheadAdder (  
    input wire [3:0] A,  
    input wire [3:0] B,  
    output wire [3:0] Sum,  
    output wire Cout  
);  
    wire [3:0] G;  
    wire [3:0] P;  
    wire [3:0] C;  
    assign G = A & B;  
    assign P = A ^ B;  
    assign C[0] = G[0] | (P[0] & Cout);  
    assign C[1] = G[1] | (P[1] & G[0]);  
    assign C[2] = G[2] | (P[2] & G[1]);  
    assign C[3] = G[3] | (P[3] & G[2]);  
    assign Sum = A ^ B ^ Cout;  
    assign Cout = C[3];  
endmodule
```

Test Bench:

```


module LookAheadAdder_TB;
    reg [3:0] A;
    reg [3:0] B;
    wire [3:0] Sum;
    wire Cout;

    CarryLookaheadAdder UUT (.A(A), .B(B), .Sum(Sum), .Cout(Cout));

    initial begin
        $display("Testing 4-Bit Carry Lookahead Adder");
        A = 4'b0000;
        B = 4'b0000;
        #10 $display("A = %b, B = %b, Sum = %b, Cout = %b", A, B, Sum, Cout);
        A = 4'b1101;
        B = 4'b1010;
        #10 $display("A = %b, B = %b, Sum = %b, Cout = %b", A, B, Sum, Cout);
        A = 4'b1111;
        B = 4'b0001;
        #10 $display("A = %b, B = %b, Sum = %b, Cout = %b", A, B, Sum, Cout);
        A = 4'b1000;
        B = 4'b1000;
        #10 $display("A = %b, B = %b, Sum = %b, Cout = %b", A, B, Sum, Cout);
        $finish;
    end
endmodule

```

RTL Schematic:

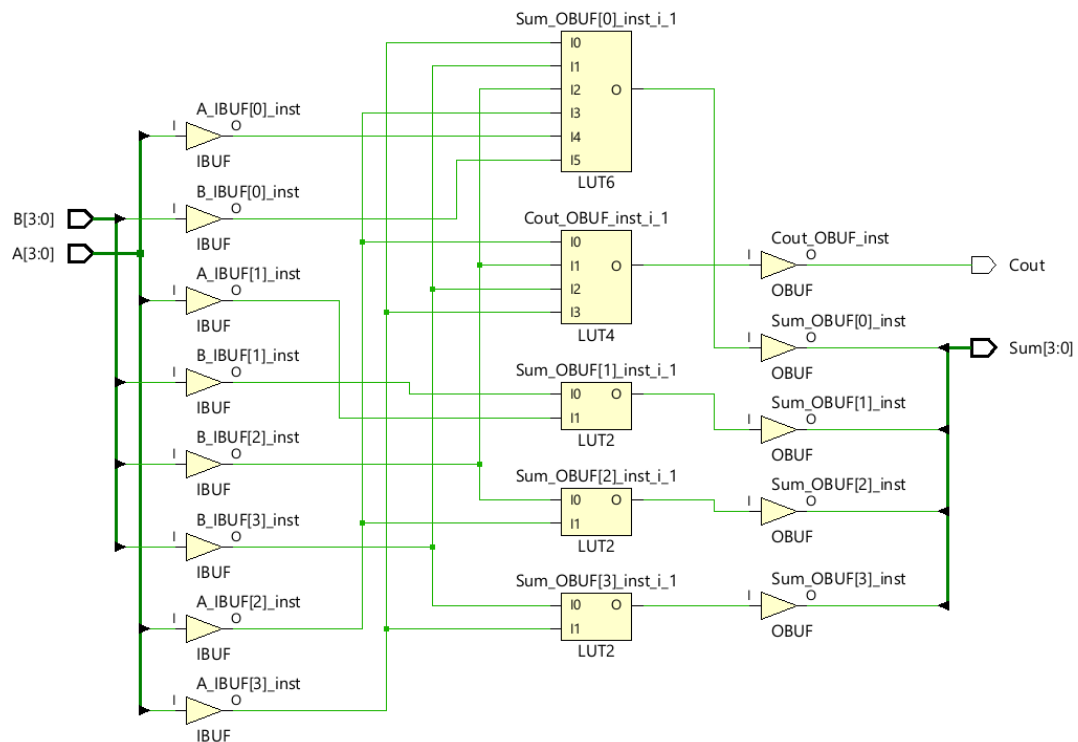

Synthesis Report:

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name | Instances |
+-----+

Report Cell Usage:
+-----+
| Cell | Count |
+-----+
| 1 | LUT2 | 3 |
| 2 | LUT4 | 1 |
| 3 | LUT6 | 1 |
| 4 | IBUF | 8 |
| 5 | OBUF | 5 |
+-----+

Report Instance Areas:
+-----+
| Instance | Module | Cells |
+-----+
| 1 | top | 18 |
+-----+

-----
Finished Writing Synthesis Report : Time (s): cpu = 00:00:16 ; elapsed = 00:00:26
```

Power Report:

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:	2.403 W
Design Power Budget:	Not Specified
Process:	typical
Power Budget Margin:	N/A
Junction Temperature:	29.5°C
Thermal Margin:	55.5°C (29.3 W)
Ambient Temperature:	25.0 °C
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

Dynamic:	2.317 W	(96%)
Device Static:	0.086 W	(4%)
Signals:	0.100 W	(4%)
Logic:	0.015 W	(1%)
I/O:	2.202 W	(95%)

9. N-Bit Comparator :-


Verilog Code:

```
module NBitComparator #(parameter N=4) (  
    input [N-1:0] A,  
    input [N-1:0] B,  
    output eq,  
    output lt,  
    output gt  
);  
    assign eq = (A == B);  
    assign lt = (A < B);  
    assign gt = (A > B);  
endmodule
```

Test Bench:

```
module testbench;  
    parameter N = 4;  
    reg [N-1:0] A;  
    reg [N-1:0] B;  
    wire eq;  
    wire lt;  
    wire gt;  
    n_bit_comparator #(N) uut (  
        .A(A),  
        .B(B),  
        .eq(eq),  
        .lt(lt),  
        .gt(gt)  
    );  
initial  
begin  
    $display("N-Bit Comparator Testbench");  
    A = 4'b0010;  
    B = 4'b0010;  
    #10 $display("A = %b, B = %b, EQ = %b, LT = %b, GT = %b", A, B, eq, lt, gt);  
    A = 4'b1100;  
    B = 4'b1010;  
    #10 $display("A = %b, B = %b, EQ = %b, LT = %b, GT = %b", A, B, eq, lt, gt);  
    A = 4'b0101;  
    B = 4'b0110;  
    #10 $display("A = %b, B = %b, EQ = %b, LT = %b, GT = %b", A, B, eq, lt, gt);  
    $finish;  
end  
endmodule
```

RTL Schematic:

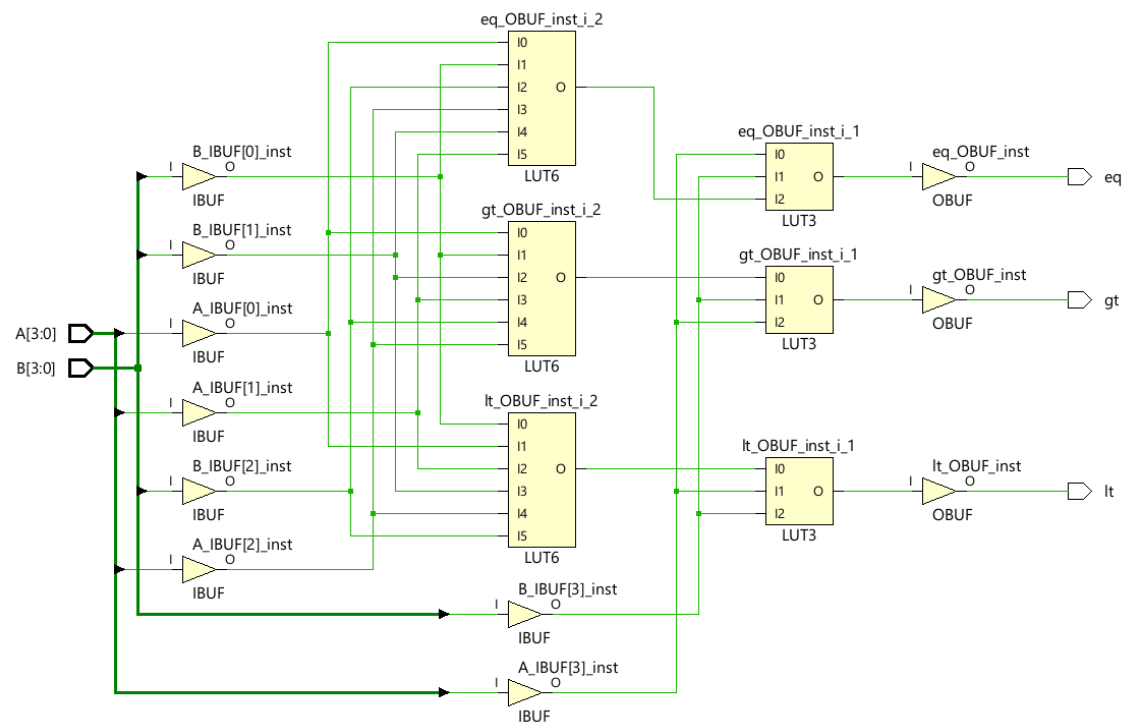

Synthesis Report:

```
-----
Start Writing Synthesis Report
-----


Report BlackBoxes:
+-----+
| BlackBox name |Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell |Count |
+-----+
|1| LUT3 | 3|
|2| LUT6 | 3|
|3| IBUF | 8|
|4| OBUF | 3|
+-----+

Report Instance Areas:
+-----+
| Instance |Module |Cells |
+-----+
|1| top | | 17|
+-----+

-----
Finished Writing Synthesis Report : Time (s): cpu = 00:00:16 ; elapsed = 00:00:26
-----
```

Power Report:

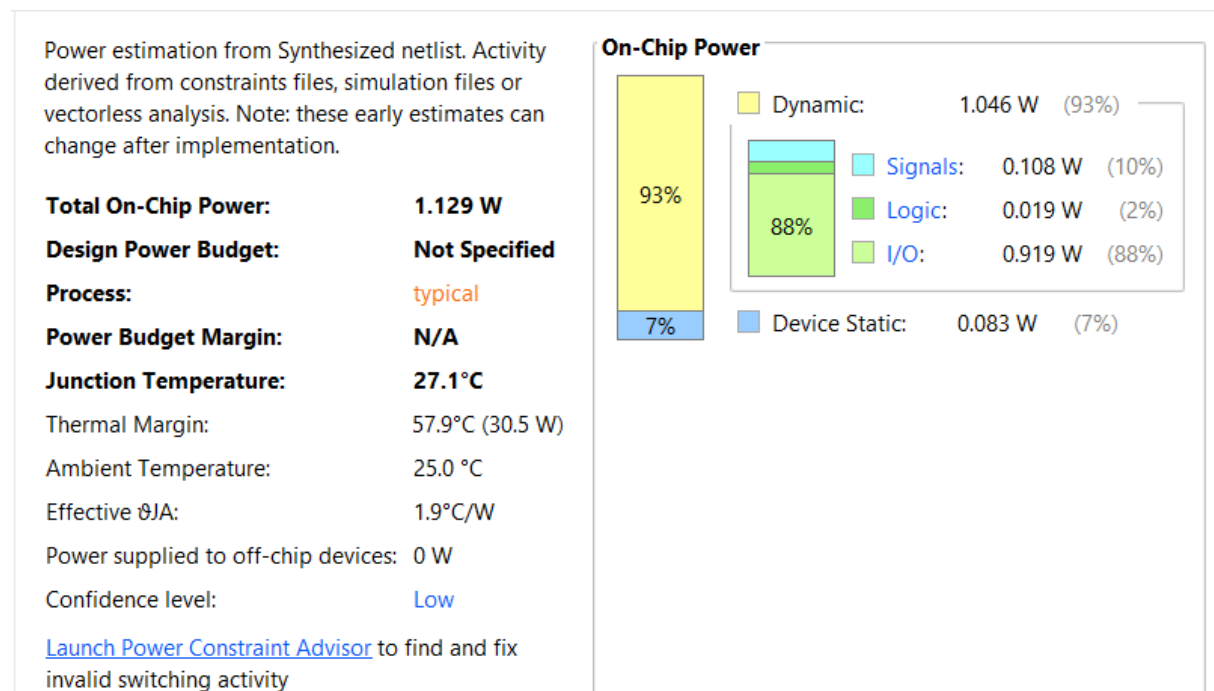

10. Serial In Serial Out Shift Register :-

Verilog Code:

```
module SISOShiftRegister #(parameter N=4) (  
    input clk,  
    input reset,  
    input serial_in,  
    output [N-1:0] serial_out  
);  
    reg [N-1:0] shift_register;  
    always @(posedge clk or posedge reset) begin  
        if (reset)  
            shift_register <= 0;  
        else  
            shift_register <= {serial_in, shift_register[N-1:1]};  
        end  
    assign serial_out = shift_register;  
endmodule
```

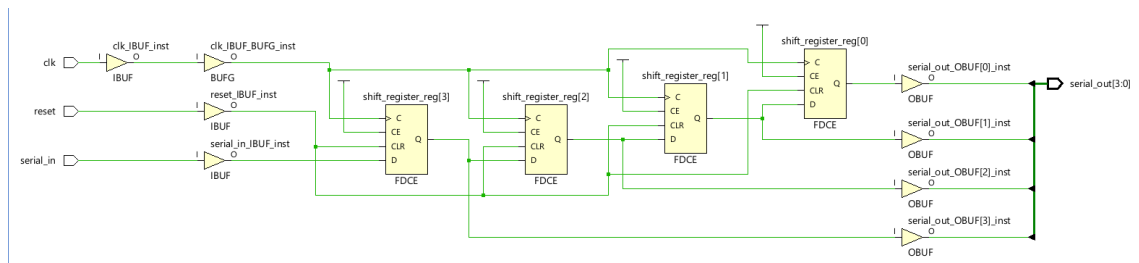

Test Bench:

```

module SISOShiftRegister_TB;
    parameter N = 4;
    parameter CLK_PERIOD = 10;
    reg clk;
    reg reset;
    reg serial_in;
    wire [N-1:0] serial_out;
    siso_shift_register #(N) uut (
        .clk(clk),
        .reset(reset),
        .serial_in(serial_in),
        .serial_out(serial_out)
    );
    always begin
        #(CLK_PERIOD / 2 ) clk = ~clk;
    end
    initial begin
        $display("SISO Shift Register Testbench");
        clk = 0;
        reset = 1;
        serial_in = 0;
        #CLK_PERIOD reset = 0;
        serial_in = 1;
        #CLK_PERIOD serial_in = 0;
        #CLK_PERIOD serial_in = 1;
        #CLK_PERIOD serial_in = 0;
        reset = 1;
        #CLK_PERIOD reset = 0;
        serial_in = 1;
        #CLK_PERIOD serial_in = 1;
        #CLK_PERIOD serial_in = 0;
        #CLK_PERIOD serial_in = 0;
        reset = 1;
        #CLK_PERIOD reset = 0;
        $display("Serial Out: %b", serial_out);
        $finish;
    end
endmodule

```

RTL Schematic:



Synthesis Report:

```
-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-+-----+-----+
| |BlackBox name |Instances |
+-+-----+-----+
+-+-----+-----+

Report Cell Usage:
+-----+-----+
|      |Cell |Count |
+-----+-----+
|1      |BUFG |    1|
|2      |FDCE |    4|
|3      |IBUF |    3|
|4      |OBUF |    4|
+-----+-----+

Report Instance Areas:
+-----+-----+-----+
|      |Instance |Module |Cells |
+-----+-----+-----+
|1      |top      |      |   12|
+-----+-----+-----+

-----
Finished Writing Synthesis Report : Time (s): cpu = 00:00:16 ; elapsed = 00:00:26
-----
```

Power Report:

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:	1.099 W
Design Power Budget:	Not Specified
Process:	typical
Power Budget Margin:	N/A
Junction Temperature:	27.1°C
Thermal Margin:	57.9°C (30.6 W)
Ambient Temperature:	25.0 °C
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

Dynamic:	1.016 W	(92%)
Device Static:	0.083 W	(8%)
Signals:	0.045 W	(4%)
Logic:	0.007 W	(1%)
I/O:	0.964 W	(95%)

11. Serial In Parallel Out Shift Register :-


Verilog Code:

```
module SIPOShiftRegister #(parameter N=4) (  
    input clk,  
    input reset,  
    input serial_in,  
    output [N-1:0] parallel_out  
);  
    reg [N-1:0] shift_register;  
    always @(posedge clk or posedge reset) begin  
        if (reset)  
            shift_register <= 0;  
        else  
            shift_register <= {shift_register[N-2:0], serial_in};  
        end  
        assign parallel_out = shift_register;  
    endmodule
```

Test Bench:

```
module SIPOShiftRegister_TB;  
    parameter N = 4;  
    parameter CLK_PERIOD = 10;  
    reg clk;  
    reg reset;  
    reg serial_in;  
    wire [N-1:0] parallel_out;  
  
    sipo_shift_register #(N) uut (  
        .clk(clk),  
        .reset(reset),  
        .serial_in(serial_in),  
        .parallel_out(parallel_out)  
    );  
    always begin  
        #(CLK_PERIOD / 2) clk = ~clk;  
    end  
    initial begin  
        $display("SIPO Shift Register Testbench");  
        clk = 0;  
        reset = 1;  
        serial_in = 0;  
        #CLK_PERIOD reset = 0;  
        serial_in = 1;  
        #CLK_PERIOD serial_in = 0;  
        #CLK_PERIOD serial_in = 1;  
        #CLK_PERIOD serial_in = 0;  
        reset = 1;  
        #CLK_PERIOD reset = 0;  
        $display("Parallel Out: %b", parallel_out);  
        $finish;  
    end  
endmodule
```

RTL Schematic:

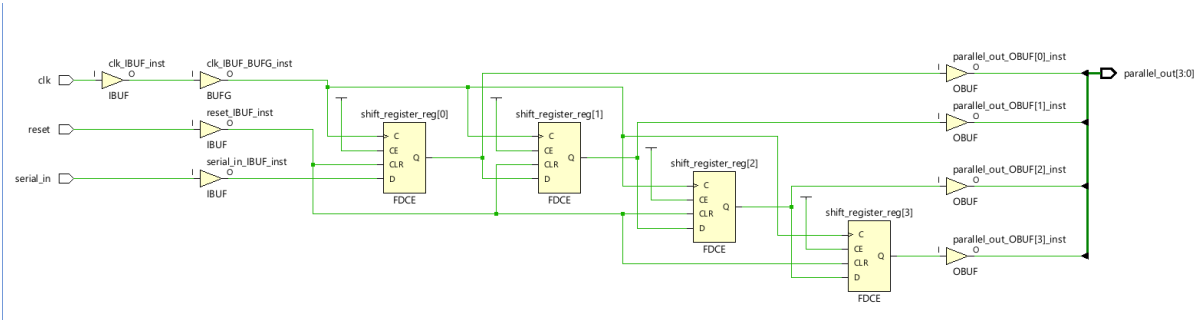

Synthesis Report:

```
-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+-----+
| BlackBox name |Instances |
+-----+-----+
+-----+-----+

Report Cell Usage:
+-----+-----+-----+
|      |Cell |Count |
+-----+-----+-----+
| 1     |BUFG |    1 |
| 2     |FDCE |    4 |
| 3     |IBUF |    3 |
| 4     |OBUF |    4 |
+-----+-----+-----+

Report Instance Areas:
+-----+-----+-----+-----+
|      |Instance |Module |Cells |
+-----+-----+-----+-----+
| 1     |top      |       |   12 |
+-----+-----+-----+-----+
-----

Finished Writing Synthesis Report : Time (s): cpu = 00:00:15 ; elapsed = 00:00:24
```


Power Report:

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: **1.099 W**
Design Power Budget: **Not Specified**
Process: **typical**
Power Budget Margin: **N/A**
Junction Temperature: **27.1°C**
Thermal Margin: 57.9°C (30.6 W)
Ambient Temperature: 25.0 °C
Effective θ_{JA} : 1.9°C/W
Power supplied to off-chip devices: 0 W
Confidence level: **Low**

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

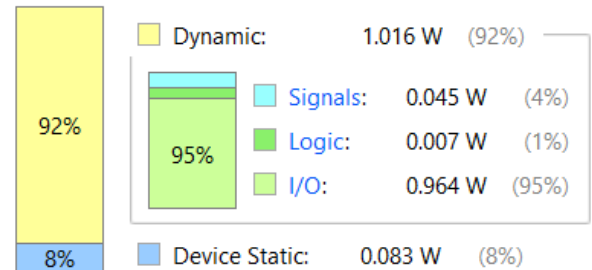

12. Parallel In Parallel Out Register :-

Verilog Code:

```
module PIPORegister #(parameter N=4) (  
    input clk,  
    input reset,  
    input [N-1:0] parallel_in,  
    output [N-1:0] parallel_out  
);  
    reg [N-1:0] shift_register;  
    always @(posedge clk or posedge reset) begin  
        if (reset)  
            shift_register <= 0;  
        else  
            shift_register <= parallel_in;  
        end  
    assign parallel_out = shift_register;  
endmodule
```


Test Bench:

```

module PIPORegister_TB;
    parameter N = 4;
    parameter CLK_PERIOD = 10;
    reg clk;
    reg reset;
    integer parallel_in;
    wire [N-1:0] parallel_out;
    pipo_shift_register #(N) uut (
        .clk(clk),
        .reset(reset),
        .parallel_in(parallel_in),
        .parallel_out(parallel_out)
    );
    always begin
        #(CLK_PERIOD / 2) clk = ~clk;
    end
    initial begin
        $display("PIPO Shift Register Testbench");
        clk = 0;
        reset = 1;
        parallel_in = 4'b0000;
        #CLK_PERIOD reset = 0;
        parallel_in = 4'b1010;
        #CLK_PERIOD parallel_in = 4'b0101;
        reset = 1;
        #CLK_PERIOD reset = 0;
        $display("Parallel Out: %b", parallel_out);
        $finish;
    end
end
endmodule

```

RTL Schematic:

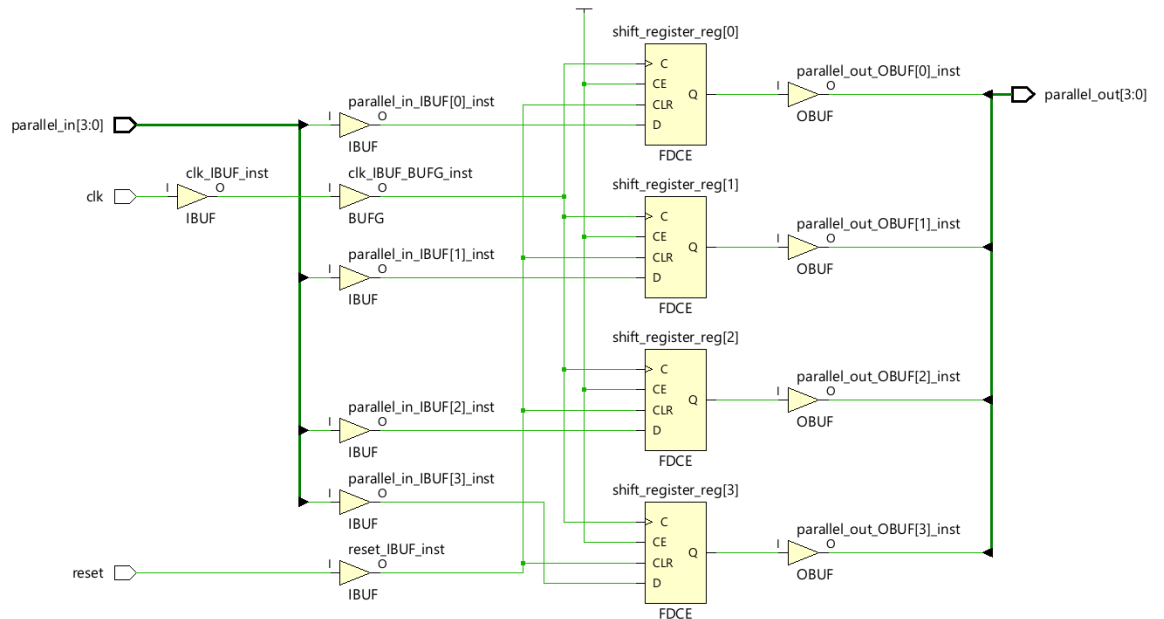

Synthesis Report:

```
-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
++-----+
| |BlackBox name |Instances |
++-----+
++-----+

Report Cell Usage:
+-----+
| |Cell |Count |
+-----+
|1 |BUFG | 1|
|2 |FDCE | 4|
|3 |IBUF | 6|
|4 |OBUF | 4|
+-----+

Report Instance Areas:
+-----+
| |Instance |Module |Cells |
+-----+
|1 |top | | 15|
+-----+


-----
Finished Writing Synthesis Report : Time (s): cpu = 00:00:15 ; elapsed = 00:00:25
-----
```

Power Report:

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:	1.106 W
Design Power Budget:	Not Specified
Process:	typical
Power Budget Margin:	N/A
Junction Temperature:	27.1°C
Thermal Margin:	57.9°C (30.6 W)
Ambient Temperature:	25.0 °C
Effective θJA:	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

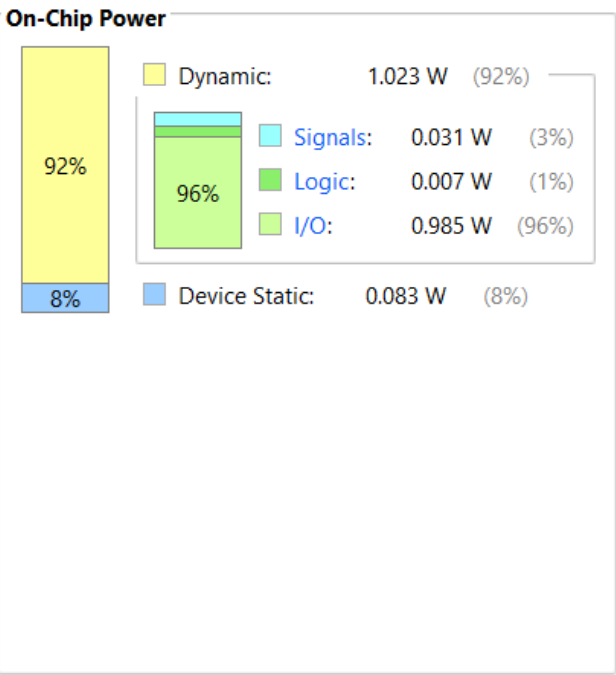[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



13. Parallel In Serial Out Register :-


Verilog Code:

```
module PISORegister #(parameter N=4) (  
    input clk,  
    input reset,  
    input [N-1:0] parallel_in,  
    output serial_out  
);  
    reg [N-1:0] shift_register;  
    reg [N-1:0] temp;  
    always @(posedge clk or posedge reset) begin  
        if (reset)  
            shift_register <= 0;  
        else  
            shift_register <= parallel_in;  
        end  
    always @(posedge clk or posedge reset) begin  
        if (reset)  
            temp <= 0;  
        else  
            temp <= {shift_register[N-2:0], temp[N-1]};  
        end  
    assign serial_out = temp[0];  
endmodule
```

Test Bench:

```
module PISORegister_TB;  
    parameter N = 4;  
    parameter CLK_PERIOD = 10;  
    reg clk;  
    reg reset;  
    integer parallel_in;  
    wire serial_out;  
    piso_shift_register #(N) uut (  
        .clk(clk),  
        .reset(reset),  
        .parallel_in(parallel_in),  
        .serial_out(serial_out)  
    );  
    always begin  
        #(CLK_PERIOD / 2) clk = ~clk;  
    end  
    initial begin  
        $display("PISO Shift Register Testbench");  
        clk = 0;  
        reset = 1;  
        parallel_in = 4'b0000;  
        #CLK_PERIOD reset = 0;  
        parallel_in = 4'b1010;  
        #CLK_PERIOD parallel_in = 4'b0101;  
        reset = 1;  
        #CLK_PERIOD reset = 0;  
        $display("Serial Out: %b", serial_out);  
        $finish;  
    end  
endmodule
```


RTL Schematic:

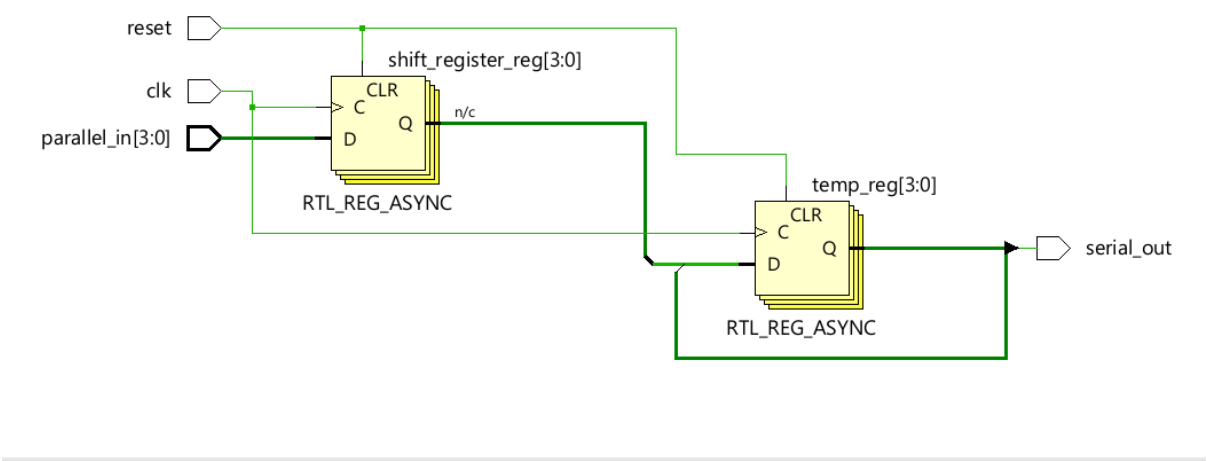

Synthesis Report:

```
-----
Start Writing Synthesis Report
-----


Report BlackBoxes:
+-----+-----+
| BlackBox name |Instances |
+-----+-----+
+-----+-----+

Report Cell Usage:
+-----+-----+
| Cell |Count |
+-----+-----+
|1| BUFG | 1|
|2| FDCE | 3|
|3| IBUF | 3|
|4| OBUF | 1|
+-----+-----+

Report Instance Areas:
+-----+-----+
| Instance |Module |Cells |
+-----+-----+
|1| top | 8|
+-----+-----+

-----
Finished Writing Synthesis Report : Time (s): cpu = 00:00:14 ; elapsed = 00:00:25
-----
```

Power Report:

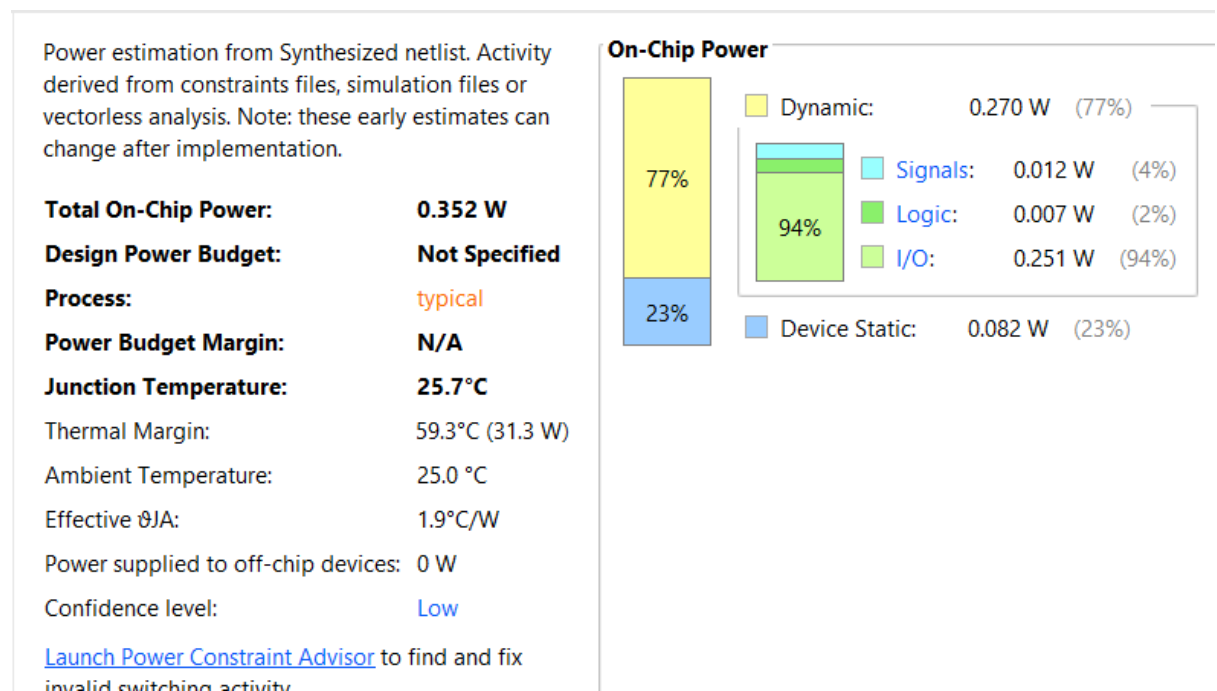

14. Bi-Direction Shift Register :-


Verilog Code:

```
module bidirectional_shift_register #(parameter N=8) (  
    input clk,  
    input reset,  
    input shift_left,  
    input shift_right,  
    input [N-1:0] parallel_in,  
    output [N-1:0] parallel_out  
);  
    reg [N-1:0] shift_register;  
    reg [N-1:0] temp;  
    always @(posedge clk or posedge reset) begin  
        if (reset)  
            shift_register <= 0;  
        else if (shift_left)  
            shift_register <= {shift_register[N-2:0], 1'b0};  
        else if (shift_right)  
            shift_register <= {1'b0, shift_register[N-1:1]};  
        else  
            shift_register <= parallel_in;  
        end  
    assign parallel_out = shift_register;  
endmodule
```

Test Bench:

```
module BidirectionRegister_TB;
    parameter N = 8;
    parameter CLK_PERIOD = 10;
    reg clk;
    reg reset;
    reg shift_left;
    reg shift_right;
    integer parallel_in;
    wire [N-1:0] parallel_out;
    bidirectional_shift_register #(N) uut (
        .clk(clk),
        .reset(reset),
        .shift_left(shift_left),
        .shift_right(shift_right),
        .parallel_in(parallel_in),
        .parallel_out(parallel_out)
    );
    always begin
        #(CLK_PERIOD / 2 ) clk = ~clk; end
    initial begin
        $display("Bidirectional Shift Register Testbench");
        clk = 0;
        reset = 1;
        shift_left = 0;
        shift_right = 0;
        parallel_in = 8'b00000000;
        #CLK_PERIOD reset = 0;
        parallel_in = 8'b10101010;
        shift_left = 1;
        #CLK_PERIOD shift_left = 0;
        shift_right = 1;
        #CLK_PERIOD shift_right = 0;
        shift_right = 1;
        #CLK_PERIOD shift_right = 0;
        parallel_in = 8'b11001100;
        shift_left = 1;
        #CLK_PERIOD shift_left = 0;
        $display("Parallel Out: %b", parallel_out);
        $finish;
    end
endmodule
```

RTL Schematic:

 

Synthesis Report:

```
-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| |BlackBox name |Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| |Cell |Count |
+-----+
|1 |BUFG | 1|
|2 |LUT4 | 2|
|3 |LUT5 | 6|
|4 |FDCE | 8|
|5 |IBUF | 12|
|6 |OBUF | 8|
+-----+

Report Instance Areas:
+-----+
| |Instance |Module |Cells |
+-----+
|1 |top | | 37|
+-----+


-----
Finished Writing Synthesis Report : Time (s): cpu = 00:00:17 ; elapsed = 00:00:27
```

Power Report:

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: **4.307 W**
Design Power Budget: **Not Specified**
Process: **typical**
Power Budget Margin: **N/A**
Junction Temperature: **33.1°C**
Thermal Margin: 51.9°C (27.4 W)
Ambient Temperature: 25.0 °C
Effective θ_{JA} : 1.9°C/W
Power supplied to off-chip devices: 0 W
Confidence level: **Low**
[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

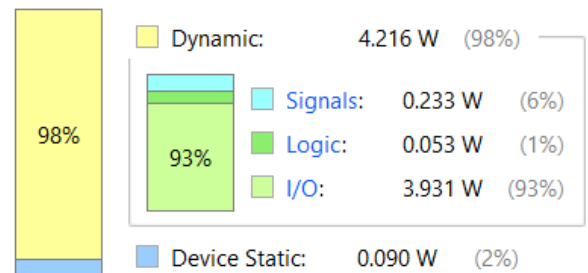

15. PRBS Sequence Generator :-


Verilog Code:

```
module PRBSsequence (
    input clk,
    input reset,
    output prbs_out
);
    reg [3:0] shift_register;
    always @(posedge clk or posedge reset) begin
        if (reset)
            shift_register <= 4'b0001;
        else
            shift_register <= {shift_register[2:0], shift_register[3] ^ shift_register[0]};
        end
    assign prbs_out = shift_register;
endmodule
```

Test Bench:

```
module PRBSsequence_TB;
    parameter CLK_PERIOD = 10;
    reg clk;
    reg reset;
    wire [3:0] prbs_out;
    integer i;
    prbs_generator uut (
        .clk(clk),
        .reset(reset),
        .prbs_out(prbs_out)
    );
    always begin
        #(CLK_PERIOD / 2) clk = ~clk;
    end
    initial begin
        $display("PRBS Generator Testbench");
        clk = 0;
        reset = 1;
        #CLK_PERIOD reset = 0;
        $display("PRBS Output:");
        for ( i = 0; i < 16; i = i + 1) begin
            #CLK_PERIOD;
            $display("%b", prbs_out);
        end
        $finish;
    end
endmodule
```

RTL Schematic:

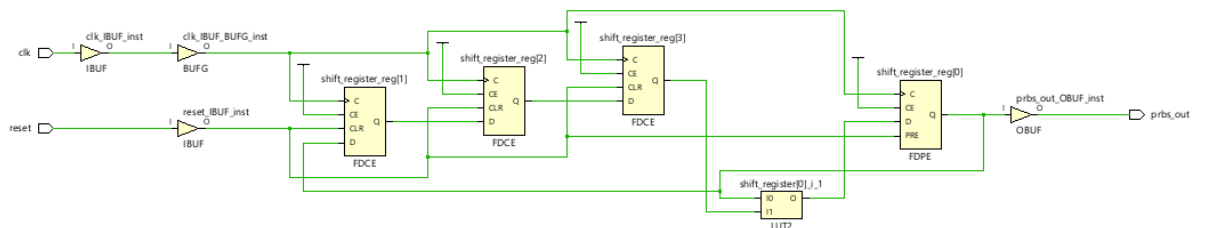

Synthesis Report:

```
-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-+-----+-----+
| |BlackBox name |Instances |
+-+-----+-----+
+-+-----+-----+

Report Cell Usage:
+-----+-----+
| |Cell |Count |
+-----+-----+
|1| |BUFG | 1|
|2| |LUT2 | 1|
|3| |FDCE | 3|
|4| |FDPE | 1|
|5| |IBUF | 2|
|6| |OBUF | 1|
+-----+-----+

Report Instance Areas:
+-----+-----+-----+
| |Instance |Module |Cells |
+-----+-----+-----+
|1| |top | | 9|
+-----+-----+-----+

-----
Finished Writing Synthesis Report : Time (s): cpu = 00:00:18 ; elapsed = 00:00:27
-----
```

Power Report:

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:	1.134 W
Design Power Budget:	Not Specified
Process:	typical
Power Budget Margin:	N/A
Junction Temperature:	27.1°C
Thermal Margin:	57.9°C (30.5 W)
Ambient Temperature:	25.0 °C
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

Dynamic:	1.051 W	(93%)
Signals:	0.076 W	(7%)
Logic:	0.018 W	(2%)
I/O:	0.957 W	(91%)
Device Static:	0.083 W	(7%)

16. 8-Bit Subtractor :-


Verilog Code:

```
module eightBitSubtractor(  
    input [7:0] A,  
    input [7:0] B,  
    input borrow_in,  
    output [7:0] difference,  
    output borrow_out  
);  
    wire [7:0] B_complement;  
    assign B_complement = (~B) + 1;  
    assign {borrow_out, difference} = A + B_complement + borrow_in;  
endmodule
```

Test Bench:

```
module eightBitSubtractor_TB;  
    reg [7:0] A;  
    reg [7:0] B;  
    reg borrow_in;  
    wire [7:0] difference;  
    wire borrow_out;  
    eight_bit_subtractor uut (  
        .A(A),  
        .B(B),  
        .borrow_in(borrow_in),  
        .difference(difference),  
        .borrow_out(borrow_out)  
    );  
    initial begin  
        $display("8-Bit Subtractor Testbench");  
        A = 8'b00001010;  
        B = 8'b00000101;  
        borrow_in = 1'b0;  
        #10 $display("A = %b, B = %b, Borrow In = %b, Difference = %b, Borrow Out = %b", A, B, borrow_in, difference, borrow_out);  
        A = 8'b00000101;  
        B = 8'b00001010;  
        borrow_in = 1'b1;  
        #10 $display("A = %b, B = %b, Borrow In = %b, Difference = %b, Borrow Out = %b", A, B, borrow_in, difference, borrow_out);  
        $finish;  
    end  
endmodule
```


RTL Schematic:

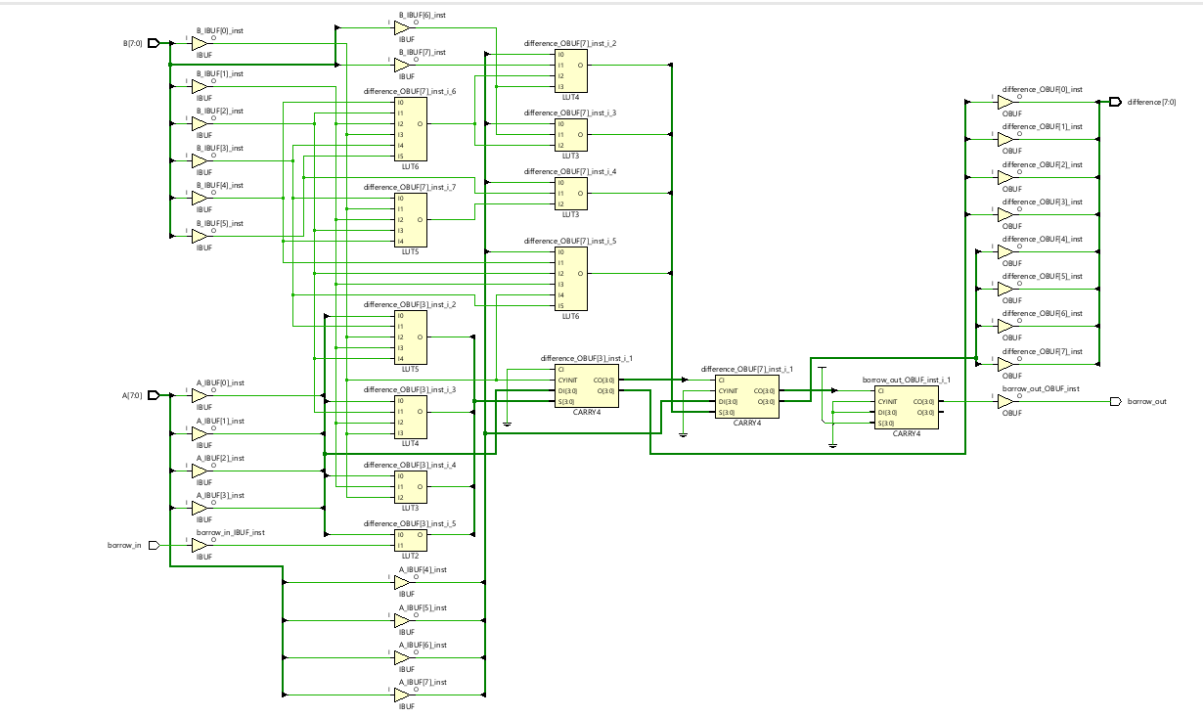

Synthesis Report:

Start Writing Synthesis Report

Report BlackBoxes:

BlackBox name	Instances
---------------	-----------

Report Cell Usage:

	Cell	Count
1	CARRY4	3
2	LUT2	1
3	LUT3	3
4	LUT4	2
5	LUT5	2
6	LUT6	2
7	IBUF	17
8	OBUF	9

Report Instance Areas:

	Instance	Module	Cells
1	top		39


Finished Writing Synthesis Report : Time (s): cpu = 00:00:18 ; elapsed = 00:00:29

Power Report:

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:	6.491 W
Design Power Budget:	Not Specified
Process:	typical
Power Budget Margin:	N/A
Junction Temperature:	37.2°C
Thermal Margin:	47.8°C (25.2 W)
Ambient Temperature:	25.0 °C
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low
Launch Power Constraint Advisor to find and fix invalid switching activity	

On-Chip Power

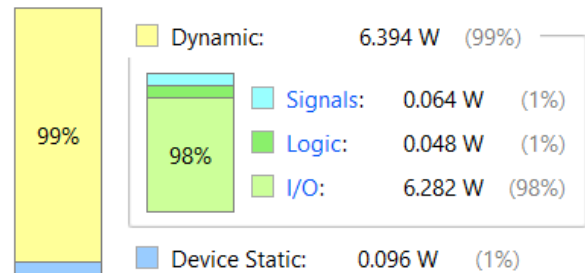

17. 8-Bit Adder/Subtractor :-


Verilog Code:

```
module eightbitAdderSubtractor(a,b,cin,sum,cout);
input [7:0] a;
input [7:0] b;
input cin;
output reg [7:0] sum;
output reg cout;
reg [8:0] c;
integer i;
always @ (a or b or cin)
begin
c[0]=cin;
if (cin == 0) begin
for ( i=0; i<8 ; i=i+1)
begin
sum[i]= a[i]^b[i]^c[i];
c[i+1]= (a[i]&b[i])|(a[i]&c[i])|(b[i]&c[i]);
end
end
else if (cin == 1) begin
for ( i=0; i<8 ; i=i+1)
begin
sum[i]= a[i]^(~ b[i])^c[i];
c[i+1]= (a[i]&(~b[i]))|(a[i]&c[i])|((~b[i])&c[i]);
end
end
cout=c[8];
end
endmodule
```

Test Bench:

```
module EightbitAdderSubtractor_TB;
    reg [7:0] A;
    reg [7:0] B;
    reg subtract;
    wire [7:0] result;
    wire overflow;
    eight_bit_adder_subtractor uut (
        .A(A),
        .B(B),
        .subtract(subtract),
        .result(result),
        .overflow(overflow)
    );
    initial begin
        $display("8-Bit Adder/Subtractor Testbench");
        A = 8'b00001010;
        B = 8'b00000101;
        subtract = 1'b0;
        #10 $display("A = %b, B = %b, Subtract = %b, Result = %b, Overflow = %b", A, B, subtract, result, overflow);
        A = 8'b00000101;
        B = 8'b00001010;
        subtract = 1'b1;
        #10 $display("A = %b, B = %b, Subtract = %b, Result = %b, Overflow = %b", A, B, subtract, result, overflow);
        $finish;
    end
endmodule
```

RTL Schematic:

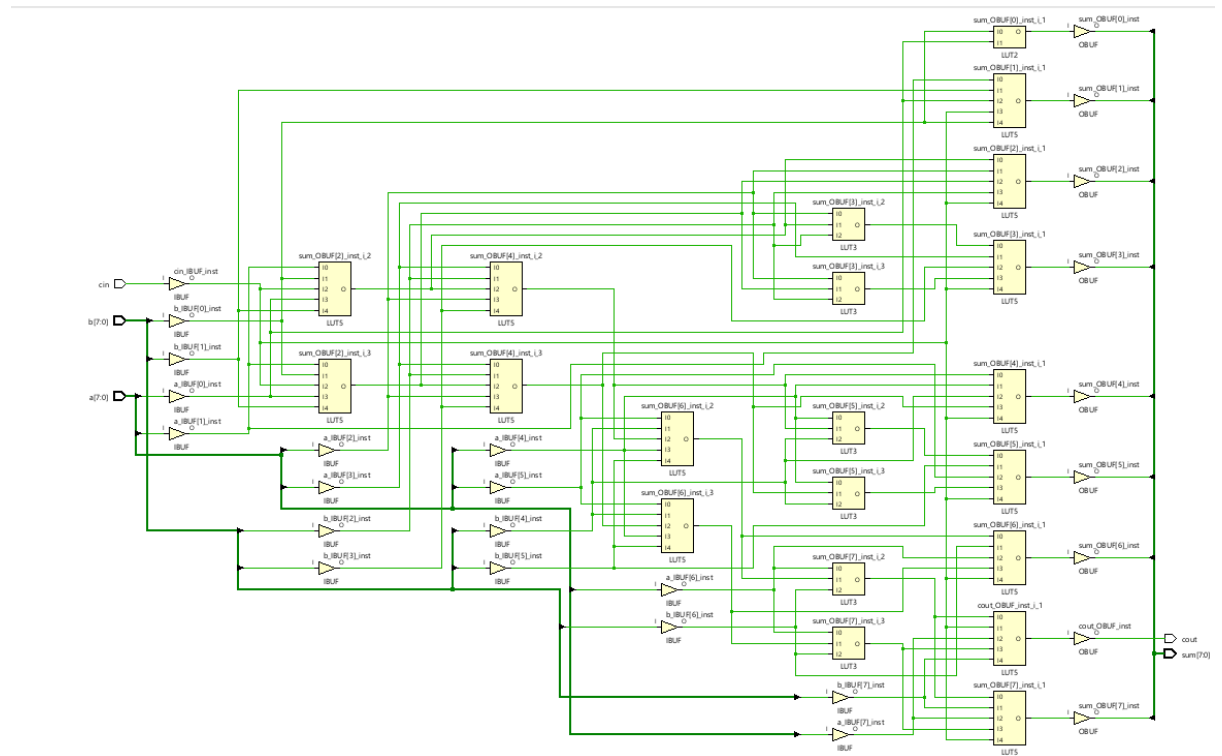

Synthesis Report:

```
-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name | Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell | Count |
+-----+
| 1 | LUT2 | 1 |
| 2 | LUT3 | 6 |
| 3 | LUT5 | 14 |
| 4 | IBUF | 17 |
| 5 | OBUF | 9 |
+-----+

Report Instance Areas:
+-----+
| Instance | Module | Cells |
+-----+
| 1 | top | | 47 |
+-----+

-----
Finished Writing Synthesis Report : Time (s): cpu = 00:00:17 ; elapsed = 00:00:35
-----
```

Power report:

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:	6.046 W
Design Power Budget:	Not Specified
Process:	typical
Power Budget Margin:	N/A
Junction Temperature:	36.4°C
Thermal Margin:	48.6°C (25.6 W)
Ambient Temperature:	25.0 °C
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

Dynamic:	5.951 W	(98%)
Device Static:	0.095 W	(2%)
Signals:	0.345 W	(6%)
Logic:	0.091 W	(2%)
I/O:	5.515 W	(92%)

18. 4-Bit Multiplier :-


Verilog Code:

```
module FourBitMultiplier (  
    input [3:0] A,  
    input [3:0] B,  
    output [7:0] product  
);  
    wire [7:0] temp_product;  
    assign temp_product = {4'b0, A} * {4'b0, B};  
    assign product = temp_product[7:0];  
endmodule
```

Test Bench:

```
module FourBitMultiplier_TB;  
    reg [3:0] A;  
    reg [3:0] B;  
    wire [7:0] product;  
    four_bit_multiplier uut (  
        .A(A),  
        .B(B),  
        .product(product)  
    );  
    initial begin  
        $display("4-Bit Multiplier Testbench");  
        A = 4'b0111;  
        B = 4'b0101;  
        #10 $display("A = %b, B = %b, Product = %b", A, B, product);  
        A = 4'b0011;  
        B = 4'b1000;  
        #10 $display("A = %b, B = %b, Product = %b", A, B, product);  
        $finish;  
    end  
endmodule
```

RTL Schematic:

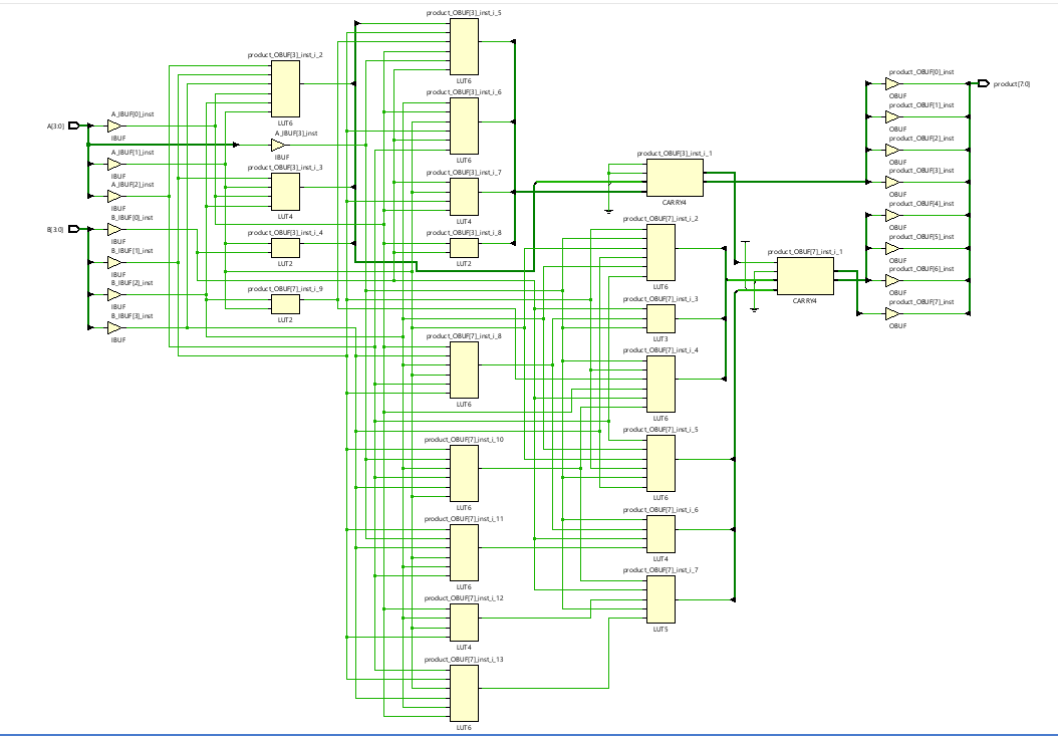

Synthesis Report:

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name |Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell |Count |
+-----+
|1| CARRY4 | 2|
|2| LUT2 | 3|
|3| LUT3 | 1|
|4| LUT4 | 4|
|5| LUT5 | 1|
|6| LUT6 | 10|
|7| IBUF | 8|
|8| OBUF | 8|
+-----+

Report Instance Areas:
+-----+
| Instance |Module |Cells |
+-----+
|1| top | | 37|
+-----+

Finished Writing Synthesis Report : Time (s): cpu = 00:00:17 ; elapsed = 00:00:24
-----
```


Power Report:

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:	4.725 W
Design Power Budget:	Not Specified
Process:	typical
Power Budget Margin:	N/A
Junction Temperature:	33.9°C
Thermal Margin:	51.1°C (26.9 W)
Ambient Temperature:	25.0 °C
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

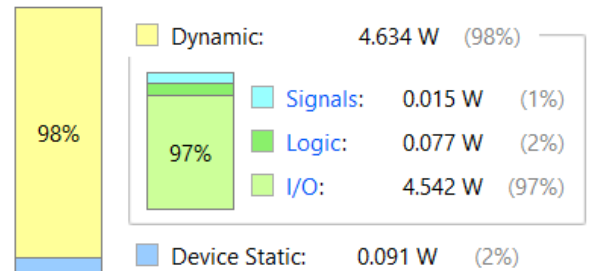

19. Fixed Point Division :-


Verilog Code:

```
module FixedPointDivision (
    input [15:0] dividend, clk, reset, divisor,
    output [15:0] quotient
);
    integer quotient;
    reg [15:0] remainder;
    reg [15:0] temp_quotient;
    reg [7:0] count;
    always @(posedge clk or posedge reset) begin
        if (reset) begin
            count <= 0;
            remainder <= 0;
            temp_quotient <= 0;
        end
        else begin
            if (remainder >= divisor) begin
                remainder <= remainder - divisor;
                temp_quotient <= temp_quotient + 1;
            end
            else begin
                remainder <= remainder;
                temp_quotient <= temp_quotient;
            end
            count <= count + 1;
            if (count == 7) begin
                quotient <= temp_quotient;
                count <= 0;
            end
        end
    end
end
endmodule
```

Test Bench:

```
module FixedPointDivision_TB;
    reg clk;
    reg reset;
    reg [15:0] dividend;
    reg [7:0] divisor;
    wire [15:0] quotient;
    fixed_point_division uut (
        .dividend(dividend),
        .divisor(divisor),
        .quotient(quotient)
    );
    always begin
        #10 clk = ~clk;
    end
    initial begin
        $display("Fixed-Point Division Testbench");
        clk = 0;
        reset = 0;
        dividend = 16'b0101100010000000;
        divisor = 8'b00000100;
        reset = 1;
        #20 reset = 0;
        dividend = 16'b0101100010000000;
        divisor = 8'b00000100;
        #20;
        $display("Dividend: %d, Divisor: %d", dividend, divisor);
        $display("Quotient: %d.%02d", quotient[15:8], quotient[7:0]);
        $finish;
    end
endmodule
```

RTL Schematic:

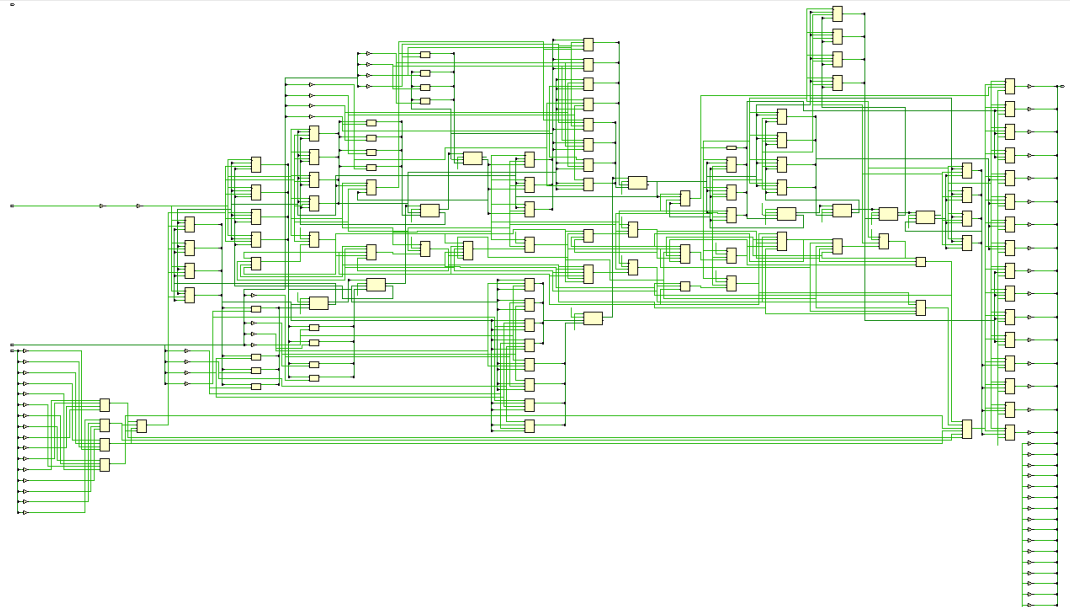

Synthesis Report:

```
-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name | Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell | Count |
+-----+
|1| BUFG | 1|
|2| CARRY4 | 10|
|3| LUT1 | 1|
|4| LUT2 | 16|
|5| LUT3 | 2|
|6| LUT4 | 23|
|7| LUT5 | 3|
|8| LUT6 | 5|
|9| FDCE | 40|
|10| FDRE | 16|
|11| IBUF | 33|
|12| OBUF | 32|
+-----+

Report Instance Areas:
+-----+
| Instance | Module | Cells |
+-----+
|1| top | | 182|
+-----+

-----
Finished Writing Synthesis Report : Time (s): cpu = 00:00:18 ; elapsed = 00:00:25
-----
```

Power Report:

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:	0.688 W
Design Power Budget:	Not Specified
Process:	typical
Power Budget Margin:	N/A
Junction Temperature:	26.3°C
Thermal Margin:	58.7°C (31.0 W)
Ambient Temperature:	25.0 °C
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

Dynamic:	0.605 W	(88%)
Device Static:	0.082 W	(12%)
Signals:	0.232 W	(38%)
Logic:	0.142 W	(23%)
I/O:	0.231 W	(39%)

20. Master Slave JK Flip Flop :-

Verilog Code:


```
module JKflipflop(
    input c,j,k,resetn,
    output Q,Qn
);
    wire MQ,MQn,Cn;
    wire j1,k1,j2,k2;
    assign j2=!resetn?0:j1;
    assign k2=!resetn?1:k2;
    and(j1,j,Qn);
    and(k1,k,Q);
    not(Cn,c);
    sr_latch master(MQ,MQn,c,j2,k2);
    sr_latch slave(Q,Qn,Cn,MQ,MQn);
endmodule

module sr_latch(
    output Q,Qn,
    input G,S,R
);
    wire S1,R1;
    and(S1,G,S);
    and(R1,G,R);
    nor(Qn,S1,Q);
    nor(Q,R1,Qn);
endmodule
```

Test Bench:

```
module JKflipflop_TB;
    reg clk;
    reg reset;
    reg J;
    reg K;
    wire Q, not_Q;
    jk_flip_flop uut (.clk(clk),.reset(reset),.J(J),.K(K),.Q(Q),.not_Q(not_Q));
    always begin
        #5 clk = ~clk;
    end
    initial begin
        $display("JK Flip-Flop Testbench");
        clk = 0;
        reset = 1;
        J = 0;
        K = 0;
        #10 reset = 0;
        J = 1;
        K = 0;
        #10;
        $display("Q = %b, ~Q = %b", Q, ~Q);
        J = 0;
        K = 1;
        #10;
        $display("Q = %b, ~Q = %b", Q, ~Q);
        J = 1;
        K = 1;
        #10;
        $display("Q = %b, ~Q = %b", Q, ~Q);
        J = 0;
        K = 0;
        #10;
        $display("Q = %b, ~Q = %b", Q, ~Q);
        $finish;
    end
endmodule
```

RTL Schematic:

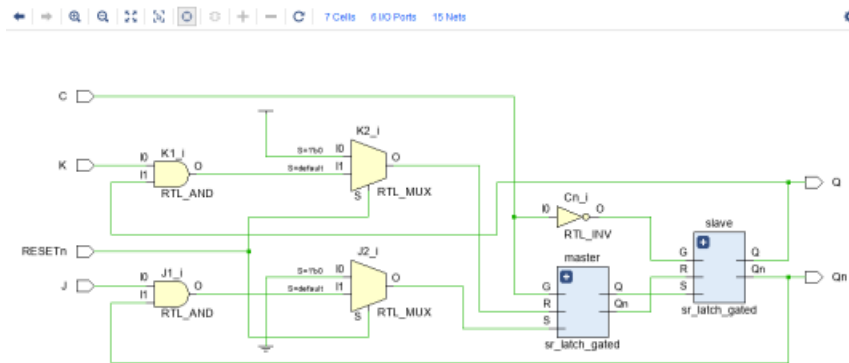

Synthesis Report:

Start Writing Synthesis Report

Report BlackBoxes:

```
+-----+
| |BlackBox name |Instances |
+-----+
+-----+
```

Report Cell Usage:


	Cell	Count
1	LUT2	1
2	LUT3	2
3	LUT6	1
4	IBUF	3
5	OBUF	2

Report Instance Areas:

```
+-----+-----+-----+
|      |Instance|Module |Cells |
+-----+-----+-----+
|1      |top      |      |    9|
+-----+-----+-----+
```

Finished Writing Synthesis Report : Time (s): cpu = 00:00:14 ; elapsed = 00:00:16

Power Report:

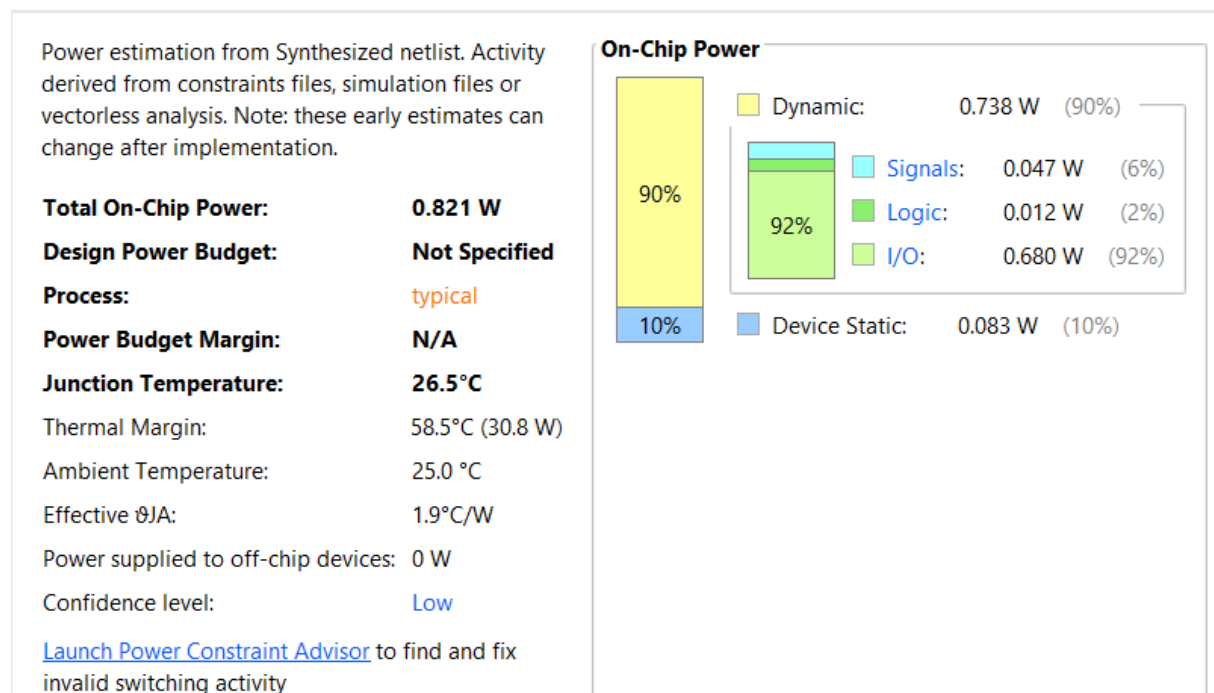

21. Positive Edge Detector :-

Verilog Code:


```
module PositiveEdgeDetector (
    input clk,
    input nreset, din,
    output dout,
    reg d_ff
);
    always @(posedge clk or negedge nreset) begin
        if (!nreset)
            d_ff <= 1'b0;
        else
            d_ff <= din;
        end
    endmodule

module d_ff(D,C,a);
    input D,C;
    output a;
    reg a;
    always@(posedge C)
    begin
        a<=D;
    end
endmodule
```

Test Bench:

```
module PositiveEdgeDetecto_TB;
    reg clk;
    reg reset;
    wire pos_edge_detected;
    positive_edge_detector uut (
        .clk(clk),
        .reset(reset),
        .pos_edge_detected(pos_edge_detected)
    );
    always begin
        #5 clk = ~clk;
    end
    initial begin
        $display("Positive Edge Detector Testbench");
        clk = 0;
        reset = 1;
        #10 reset = 0;
        #5 clk = 1;
        #5 clk = 0;
        #5 clk = 1;
        #5 clk = 0;
        $display("Positive Edge Detected: %b", pos_edge_detected);
        $finish;
    end
endmodule
```

RTL Schematic:

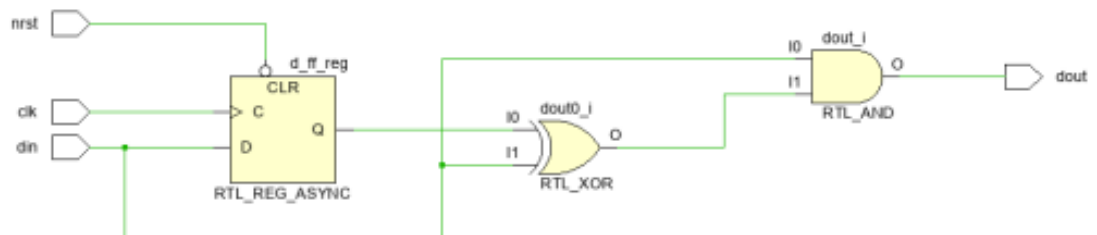

Synthesis Report:

```
-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name | Instances |
+-----+

Report Cell Usage:
+-----+
| Cell | Count |
+-----+
|1| BUFG | 1|
|2| LUT1 | 1|
|3| FDCE | 1|
|4| IBUF | 3|
|5| OBUF | 1|
|6| OBUFT | 1|
+-----+

Report Instance Areas:
+-----+
| Instance | Module | Cells |
+-----+
|1| top | | 8|
+-----+

-----
Finished Writing Synthesis Report : Time (s): cpu = 00:00:13 ; elapsed = 00:00:15
-----
```

Power Report:

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: **0.347 W**

Design Power Budget: **Not Specified**

Process: **typical**

Power Budget Margin: **N/A**

Junction Temperature: **25.7°C**

Thermal Margin: 59.3°C (31.3 W)


Ambient Temperature: 25.0 °C

Effective θ_{JA} : 1.9°C/W

Power supplied to off-chip devices: 0 W

Confidence level: **Low**

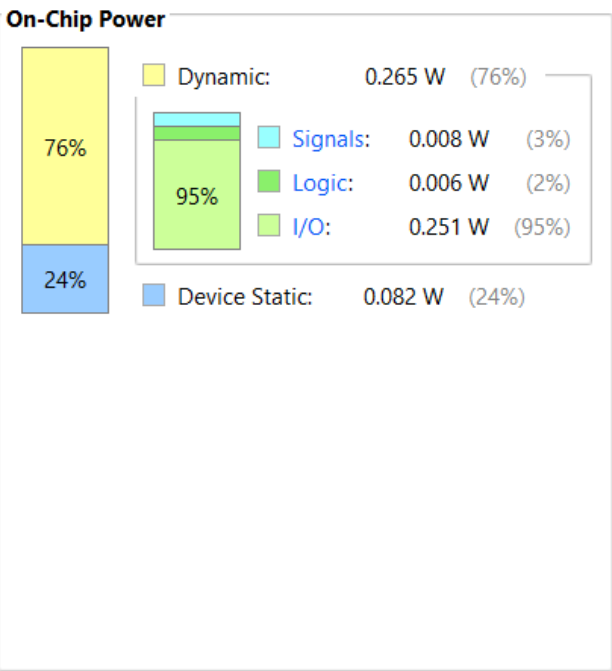[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



22. BCD Adder :-


Verilog Code:

```
module BCDAdder (
    input [3:0] A,
    input [3:0] B,
    output [3:0] sum,
    output carry_out
);
    integer sum;
    wire [3:0] sum_internal;
    wire carry_out_internal;
    assign {carry_out_internal, sum_internal} = A + B;
    assign carry_out = (sum_internal > 9);
    always @(sum_internal) begin
        if (carry_out_internal)
            sum = sum_internal + 6;
        else
            sum = sum_internal;
    end
endmodule
```

Test Bench:

```
module BCDAdder_TB;
    reg [3:0] A;
    reg [3:0] B;
    wire [3:0] sum;
    wire carry_out;
    bcd_adder uut (
        .A(A),
        .B(B),
        .sum(sum),
        .carry_out(carry_out)
    );
    initial begin
        $display("BCD Adder Testbench");
        A = 4'b0101;
        B = 4'b0011;
        #10;
        $display("A = %d, B = %d, Sum = %d, Carry Out = %b", A, B, sum, carry_out);
        A = 4'b1001;
        B = 4'b1001;
        #10;
        $display("A = %d, B = %d, Sum = %d, Carry Out = %b", A, B, sum, carry_out);
        $finish;
    end
endmodule
```

RTL Schematic:

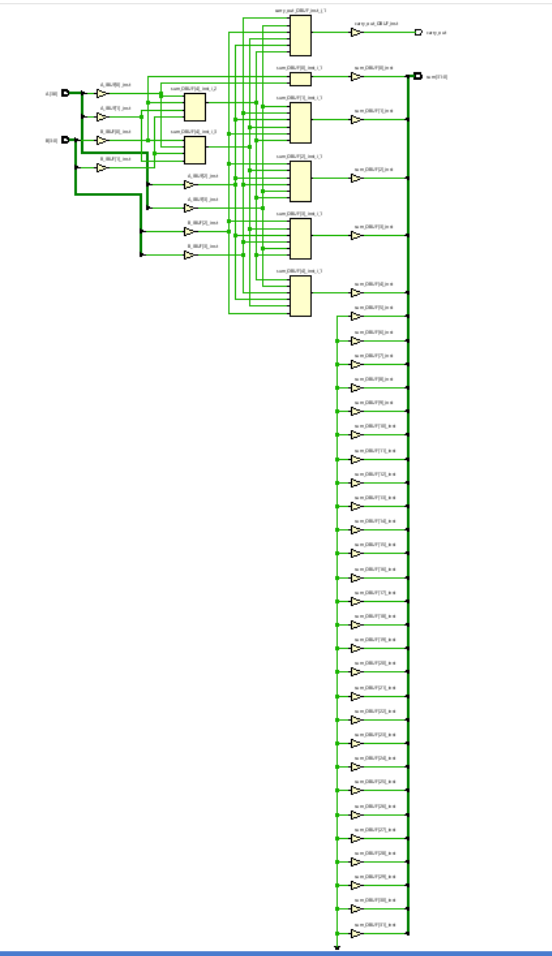

Synthesis Report;

```
-----
Start Writing Synthesis Report
-----


Report BlackBoxes:
+-----+
| BlackBox name | Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell | Count |
+-----+
| 1 | LUT2 | 1 |
| 2 | LUT4 | 2 |
| 3 | LUT6 | 5 |
| 4 | IBUF | 8 |
| 5 | OBUF | 33 |
+-----+

Report Instance Areas:
+-----+
| Instance | Module | Cells |
+-----+
| 1 | top | | 49 |
+-----+

Finished Writing Synthesis Report : Time (s): cpu = 00:00:14 ; elapsed = 00:00:16
-----
```


Power Report:

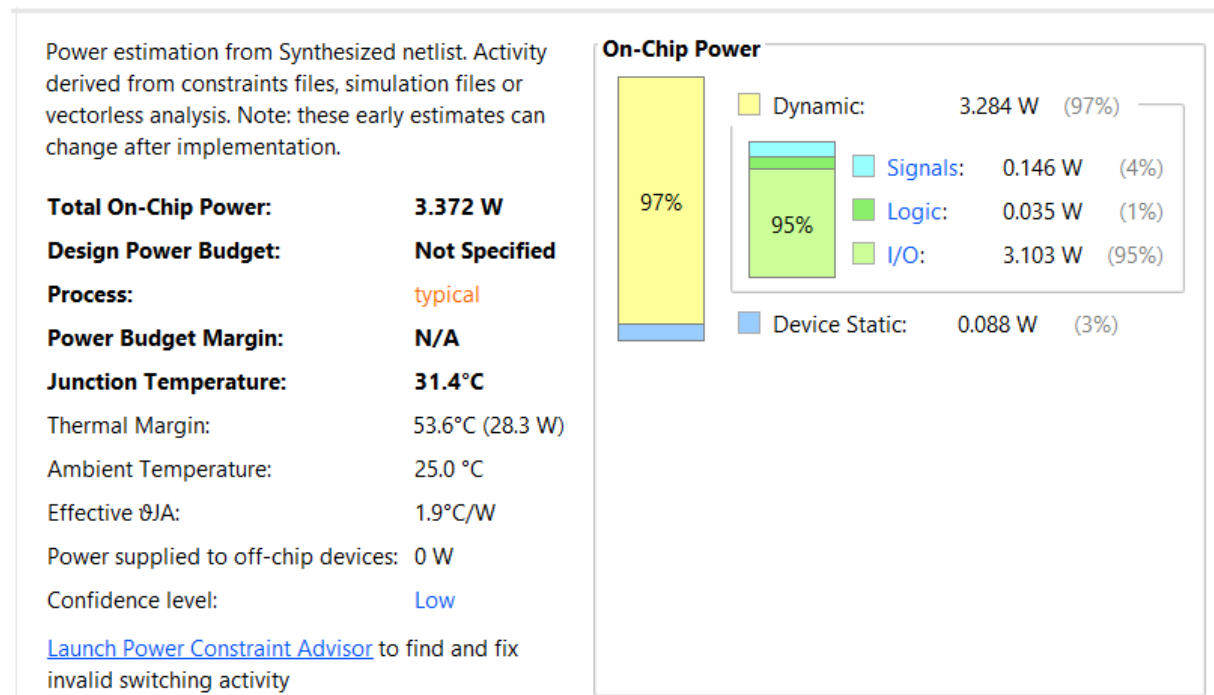

23. 4-Bit Carry Select Adder :-

Verilog Code:

```
> module CarrySelectAdder (
    input [3:0] A,
    input [3:0] B,
    input carry_in,
    output carry_out,
    output [3:0] s;
    wire [3:0] temp0, temp1;
    wire [3:0] carry0, carry1;
    fulladder fa00(A[0],B[0],1'b0,temp0[0],carry0[0]);
    fulladder fa01(A[1],B[1],carry0[0],temp0[1],carry0[1]);
    fulladder fa02(A[2],B[2],carry0[1],temp0[2],carry0[2]);
    fulladder fa03(A[3],B[3],carry0[2],temp0[3],carry0[3]);

    fulladder fa10(A[0],B[0],1'b0,temp1[0],carry1[0]);
    fulladder fa11(A[1],B[1],carry1[0],temp1[1],carry1[1]);
    fulladder fa12(A[2],B[2],carry1[1],temp1[2],carry1[2]);
    fulladder fa13(A[3],B[3],carry1[2],temp1[3],carry1[3]);

    multiplexer mux_carry (carry0[3],carry1[3],cin,cout);
    multiplexer mux_sum0(temp0[0],temp1[0],cin,s[0]);
    multiplexer mux_sum1(temp0[1],temp1[1],cin,s[1]);
    multiplexer mux_sum2(temp0[2],temp1[2],cin,s[2]);
    multiplexer mux_sum3(temp0[3],temp1[3],cin,s[3]);
> endmodule
> module fulladder(
    input a,b,cin,
    output sum,carry;
    assign sum=a^b^cin;
    assign carry=(a&b) | (cin&a) | (b&cin);
> endmodule
> module multiplexer(
    input i0,i1,sel,
    output reg bitout;
> always@(i0,i1,sel)
> begin
> if(sel==0)
>     bitout=i0;
> else
>     bitout=i1;
> end
> endmodule
```


Test Bench:

```

module CarrySelectAdder_TB;
    reg [3:0] A;
    reg [3:0] B;
    reg carry_in;
    wire [3:0] sum;
    wire carry_out;
    carry_select_adder_4bit uut (
        .A(A),
        .B(B),
        .carry_in(carry_in),
        .sum(sum),
        .carry_out(carry_out)
    );
    initial begin
        $display("4-Bit Carry-Select Adder Testbench");
        A = 4'b0111;
        B = 4'b0011;
        carry_in = 1'b0;
        #10;
        $display("A = %d, B = %d, Sum = %d, Carry Out = %b", A, B, sum, carry_out);
        A = 4'b1010;
        B = 4'b0110;
        carry_in = 1'b1;
        #10;
        $display("A = %d, B = %d, Sum = %d, Carry Out = %b", A, B, sum, carry_out);
        $finish;
    end
endmodule

```

RTL Schematic:

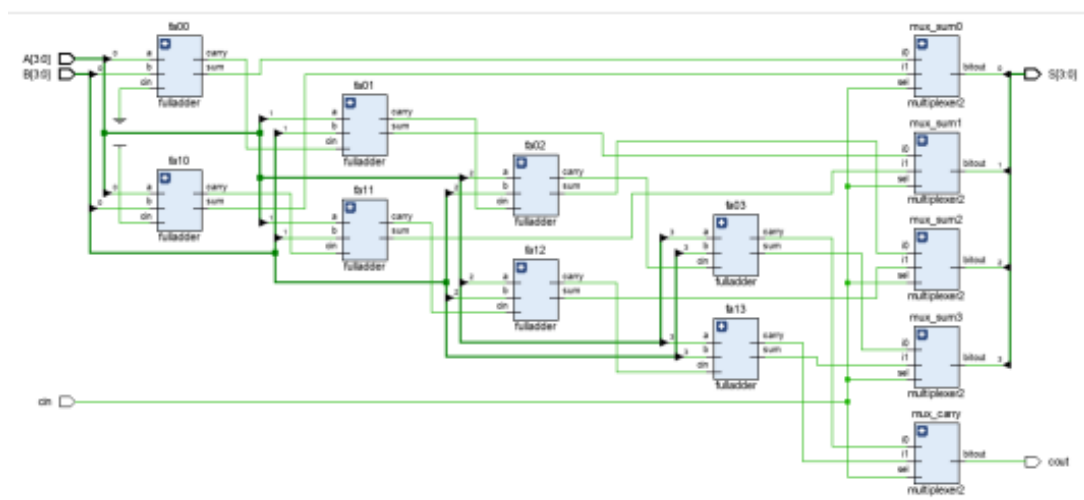

Synthesis Report:

```
-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+-----+
| |BlackBox name |Instances |
+-----+-----+
+-----+-----+

Report Cell Usage:
+-----+-----+
| |Cell |Count |
+-----+-----+
|1 |LUT2 | 1|
|2 |LUT4 | 2|
|3 |LUT5 | 1|
|4 |LUT6 | 1|
|5 |IBUF | 8|
|6 |OBUF | 4|
|7 |OBUFT | 1|
+-----+-----+

Report Instance Areas:
+-----+-----+-----+
| |Instance |Module |Cells |
+-----+-----+-----+
|1 |top | | 18|
+-----+-----+-----+

-----
Finished Writing Synthesis Report : Time (s): cpu = 00:00:13 ; elapsed = 00:00:20
```

Power Report:

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:

2.443 W

Design Power Budget:

Not Specified

Process:

typical

Power Budget Margin:

N/A

Junction Temperature:

29.6°C

Thermal Margin:

55.4°C (29.2 W)

Ambient Temperature:

25.0 °C

Effective θ JA:

1.9°C/W

Power supplied to off-chip devices:

0 W

Confidence level:

Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

96%

Dynamic: 2.357 W (96%)

94%

Signals: 0.128 W (5%)

Logic: 0.018 W (1%)

I/O: 2.211 W (94%)

Device Static: 0.086 W (4%)

24. Moore FSM 1010 Sequence Detector :-


Verilog Code:

```
module FSMSequenceDetector (
    input clk,
    input reset,
    input d_in,
    output reg y
);
    reg [2:0] cst,nst;
    parameter s0=3'b000,
               s1=3'b001,
               s2=3'b010,
               s3=3'b100,
               s4=3'b101;
    always@(cst or d_in)
    begin
        case(cst)
        s0:if(d_in==1'b1)
            begin
                nst=s1;
                y=1'b0;
            end
        else cst=nst;
        s1:if(d_in==1'b0)
            begin
                nst=s2;
                y=1'b0;
            end
        else cst=nst;
        s2:if(d_in==1'b1)
            begin
                nst=s3;
                y=1'b0;
            end
        else
            begin
                nst=s0;
                y=1'b0;
            end
        s3:if(d_in==1'b0)
            begin
                nst=s2;
                y=1'b1;
            end
        else
            begin
                nst=s1;
                y=1'b0;
            end
        default nst=s0;
        endcase
    end
    always@(posedge clk) begin
        if(reset)
            cst<=s0;
        else
            cst<=nst;
        end
    end
endmodule
```

Test Bench:

```
) module FSMSequenceDetector_TB;
    reg clk;
    reg reset;
    reg data_in;
    wire sequence_detected;
    moore_sequence_detector uut (.clk(clk),.reset(reset),.data_in(data_in),.sequence_detected(sequence_detected));
) always begin
    #5 clk = ~clk;
) end
) initial begin
    $display("Moore Sequence Detector Testbench");
    clk = 0;
    reset = 1;
    data_in = 0;
    #10 reset = 0;
    data_in = 1;
    #10 data_in = 0;
    #10 data_in = 1;
    #10 data_in = 0;
    #10 $display("Input Sequence: 1010, Sequence Detected: %b", sequence_detected);
    data_in = 1;
    #10 data_in = 1;
    #10 data_in = 1;
    #10 data_in = 0;
    #10 $display("Input Sequence: 1110, Sequence Detected: %b", sequence_detected);
    data_in = 1;
    #10 data_in = 0;
    #10 data_in = 0;
    #10 data_in = 1;
    #10 data_in = 0;
    #10 data_in = 0;
    #10 data_in = 1;
    #10 data_in = 0;
    #10 $display("Input Sequence: 10010010, Sequence Detected: %b", sequence_detected);
    $finish;
) end
) endmodule
```

RTL Schematic:

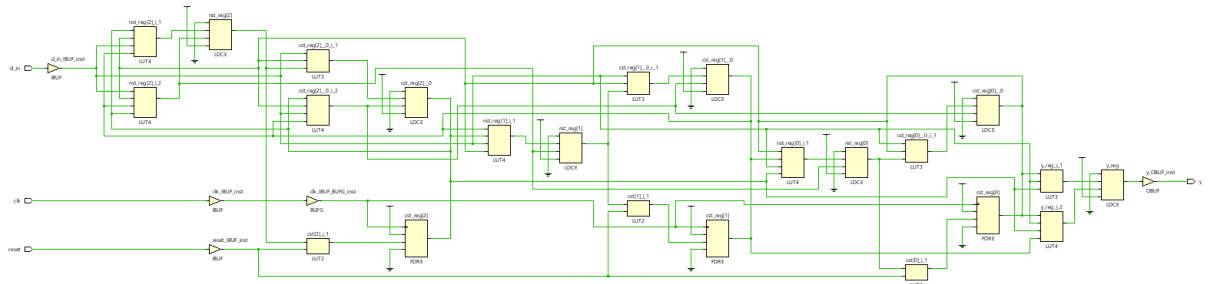

Synthesis Report:

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name |Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell |Count |
+-----+
|1| BUFG | 1|
|2| LUT2 | 3|
|3| LUT3 | 4|
|4| LUT4 | 6|
|5| FDRE | 3|
|6| LD | 7|
|7| IBUF | 3|
|8| OBUF | 1|
+-----+

Report Instance Areas:
+-----+
| Instance |Module |Cells |
+-----+
|1| top | | 28|
+-----+

-----
Finished Writing Synthesis Report : Time (s): cpu = 00:00:13 ; elapsed = 00:00:16
-----
```

Power Report:

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:	0.175 W
Design Power Budget:	Not Specified
Process:	typical
Power Budget Margin:	N/A
Junction Temperature:	25.3°C
Thermal Margin:	59.7°C (31.5 W)
Ambient Temperature:	25.0 °C
Effective θJA:	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

Dynamic:	0.094 W	(54%)
Device Static:	0.081 W	(46%)

23%	Signals:	0.021 W	(23%)
24%	Logic:	0.022 W	(24%)
53%	I/O:	0.050 W	(53%)

25. N:1 Mux :-


Verilog Code:

```
module Nx1mux(  
    input [1:0] sel,  
    input i0,i1,i2,i3,  
    output reg y );  
always@(*)begin  
    case(sel)  
        2'h0:y=i0;  
        2'h1:y=i1;  
        2'h2:y=i2;  
        2'h3:y=i3;  
        default:$display("Invalid Input");  
    endcase  
end  
endmodule
```

Test Bench:

```
module Nx1Mux_TB;  
    parameter N = 4;  
    reg [N-1:0] inputs;  
    reg select;  
    wire out;  
    n_to_1_mux #(N) uut (  
        .inputs(inputs),  
        .select(select),  
        .out(out)  
    );  
    initial begin  
        $display("N:1 MUX Testbench");  
        inputs = 4'b0000;  
        for (select = 0; select < N; select = select + 1) begin  
            $display("Select = %b, Output = %b", select, out);  
        end  
        inputs = 4'b1101;  
        for (select = 0; select < N; select = select + 1) begin  
            $display("Select = %b, Output = %b", select, out);  
        end  
        $finish;  
    end  
endmodule
```

RTL Schematic:

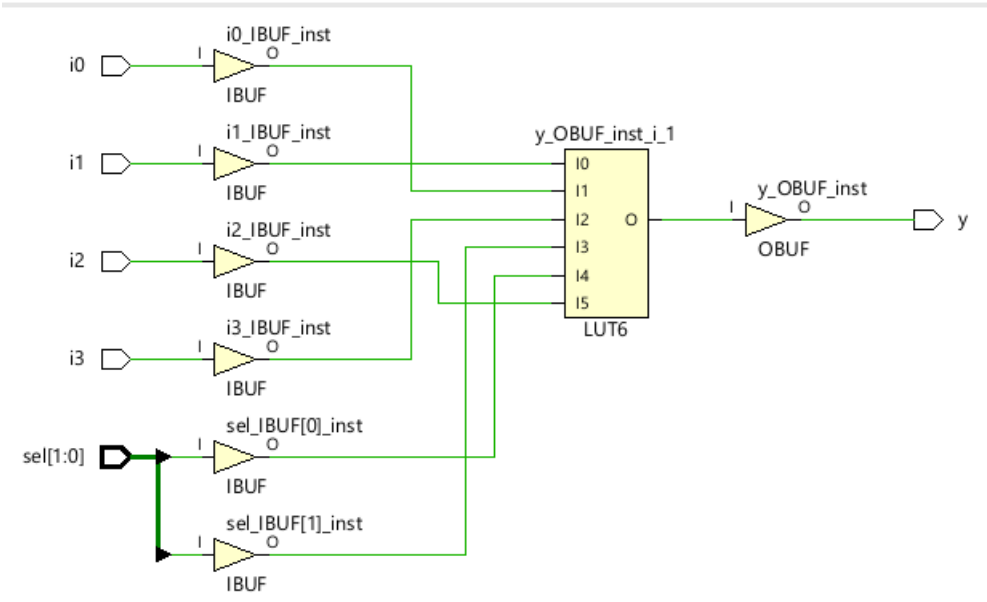

Synthesis Report:

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-+-----+-----+
| |BlackBox name |Instances |
+-+-----+-----+
+-+-----+-----+

Report Cell Usage:
+-----+-----+
|      |Cell |Count |
+-----+-----+
|1      |LUT6 |    1|
|2      |IBUF |    6|
|3      |OBUF |    1|
+-----+-----+

Report Instance Areas:
+-----+-----+-----+
|      |Instance |Module |Cells |
+-----+-----+-----+
|1      |top      |      |    8|
+-----+-----+-----+

-----
Finished Writing Synthesis Report : Time (s): cpu = 00:00:13 ; elapsed = 00:00:16
```


Power Report:

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:	0.544 W
Design Power Budget:	Not Specified
Process:	typical
Power Budget Margin:	N/A
Junction Temperature:	26.0°C
Thermal Margin:	59.0°C (31.1 W)
Ambient Temperature:	25.0 °C
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

